

## Digital Circuits: Homeworks #3

Due on Thursday, April 27, 2017

Note: Late homework is not accepted. Good luck.

### 1. Logic Circuit.

Implement a logic circuit for the following truth table.


$A$	$B$	$C$	$X$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

### 2. Adder and Subtractor.

The circuit shown in Figure 1 is a 4-bit circuit that can add or subtract numbers in a form used in computers (positive numbers in true form; negative numbers in 1's complement form).

- (a) Explain what happens when the  $\overline{Add/Subt}$  input is HIGH?
- (b) Explain what happens when the  $\overline{Add/Subt}$  input is LOW?


Figure 1: Adder and Subtractor.

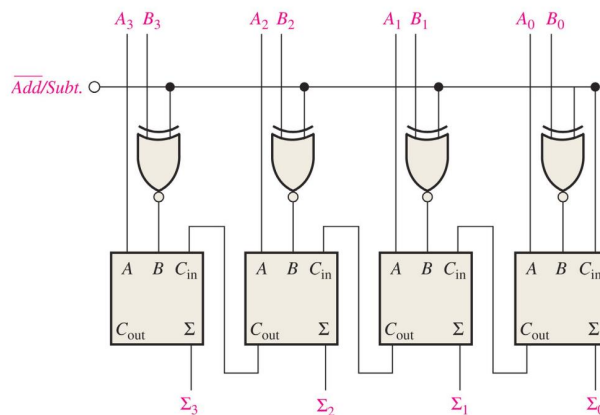

### 3. Decoder.

If the input waveforms are applied to the decoding logic as indicated in Figure 2, sketch the output waveform in proper relation to the inputs.

Figure 2: Decoder.

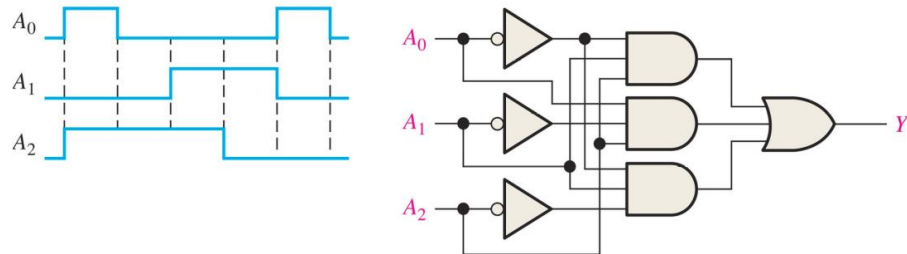

### 4. Multiplexer.

For the multiplexer in Figure 3, input states are given by  $D_0 = 1, D_1 = 0, D_2 = 0, D_3 = 1$ . Then, determine the output waveform when the data-select inputs are sequenced as shown by the waveforms in Figure 4.

Figure 3: Multiplexer.

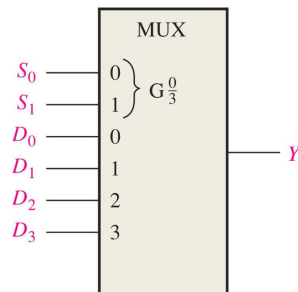


Figure 4: Data-Select Input Waveforms.

