

Digital Circuits: Homeworks #4

Due on Friday, May 26, 2017

Note: Late homework is not accepted. Good luck.

1. Gated S-R Latch.

For a gated S-R latch, draw the Q and \bar{Q} outputs for the inputs in Figure 1. Show them in proper relation to the enable input. Assume that Q starts LOW.

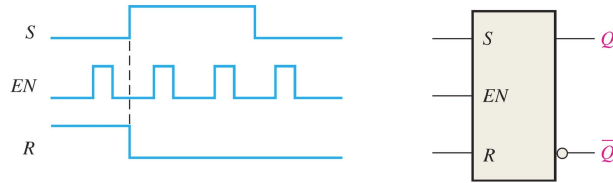


Figure 1: Input Waveform.

2. Gated D Latch.

Determine the output of a gated D latch for the inputs in Figure 2. Assume that Q starts LOW.



Figure 2: Input Waveform.

3. J-K Flip-Flops.

Two edge-triggered J-K flip-flops are shown in Figure 3. If the inputs are as shown, draw the Q output of each flip-flop relative to the clock, and explain the difference between the two. Assume that flip-flops are initially RESET.

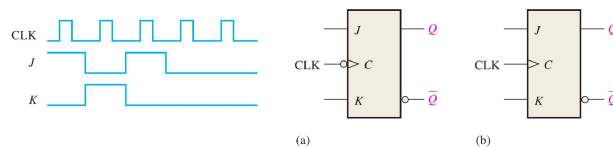


Figure 3: Input Waveform.

4. D Flip-Flops.

A D flip-flop is connected as shown in Figure 4. Draw the Q output in relation to the clock when the flip-flop is initially RESET. What specific function does this device perform?

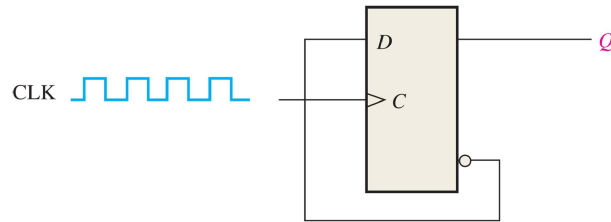


Figure 4: Input Waveform.