

Digital Circuits: Homeworks #5

Due on Wednesday, June 7, 2017

Note: Late homework is not accepted. Good luck.

1. Shift Register Data I/Os.

For the data input and clock in Figure 1a, determine the states of each flip-flop in the shift register of Figure 1b and show the Q waveforms. Assume that the register contains all 1s initially.

 


Figure 1: Input Waveform and Serial In/Serial Out Shift Register.

2. Bidirectional Shift Registers.

Determine the state of the shift register of Figure 2b after each clock pulse for the given $RIGHT/LEFT$ control input waveform in Figure 2a. Assume that $Q_0 = 0$, $Q_1 = 1$, $Q_2 = 1$, $Q_3 = 0$, and that the serial data-input line is HIGH.

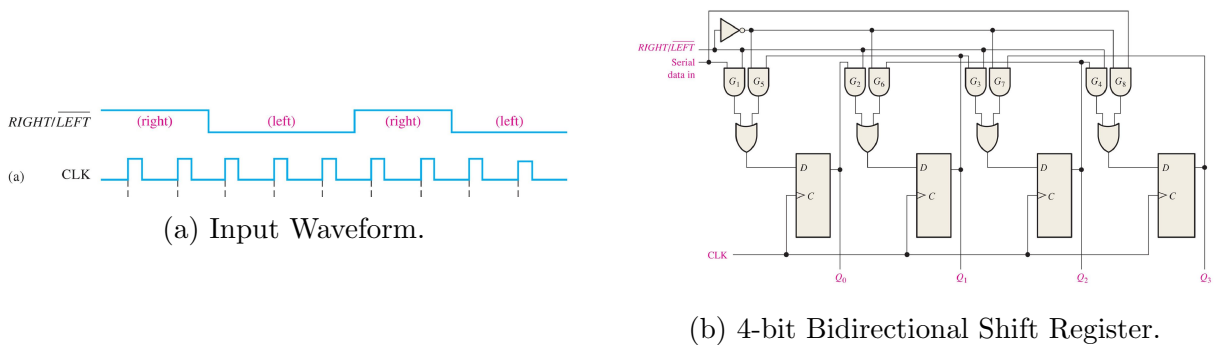


Figure 2: 4-bit Bidirectional Shift Register and Input Waveform.

3. Synchronous Counters.

Determine the sequence of the counter in Figure 3. Show the complete timing diagram of Q_0 , Q_1 , and Q_2 waveforms for 10 clock pulses. Begin with the counter cleared.

 


Figure 3: Synchronous Counter.

4. Design of Synchronous Counters.

Design a counter to produce the following binary sequence using J-K flip-flops.

1, 4, 3, 5, 7, 6, 2, 1, 4, 3, 5,

Please follow 6 steps to design the counter.

(Hint: We have 7 states from 001 to 111. You can start from drawing the state diagram.)

(Hint2: Use don't care when the present state is 000.)