

# Digital Fundamentals


Thomas L. Floyd

Combinational Logic Analysis

**Chapter 5**

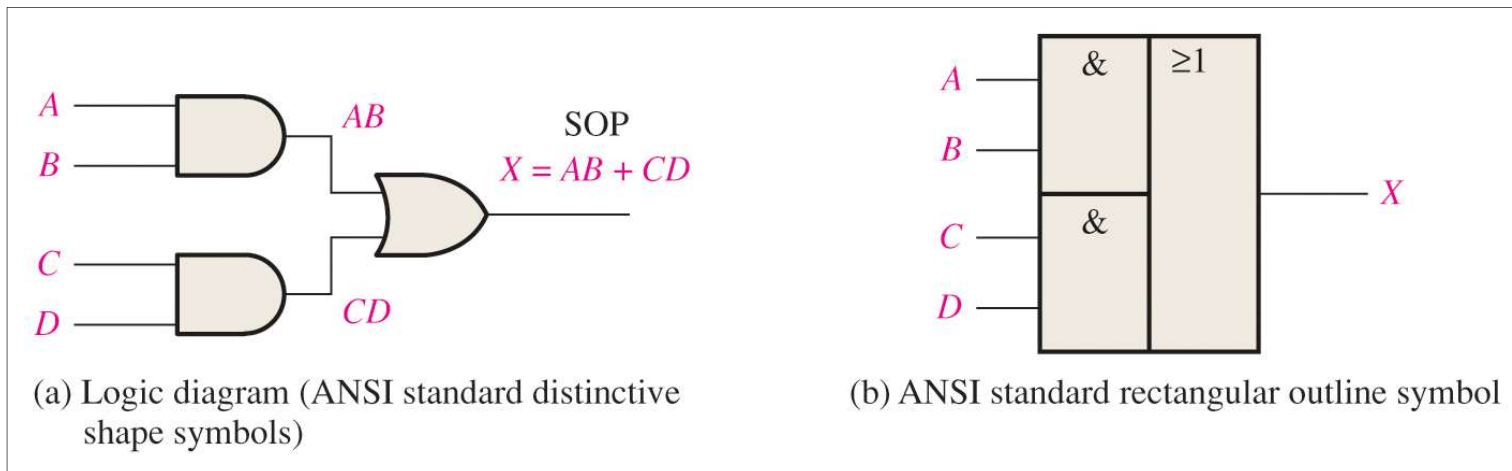
# Combinational Logic Circuits

In Sum-of-Products (SOP) form, basic combinational circuits can be directly implemented with AND-OR combinations if the necessary complement terms are available.



# Combinational Logic Circuit Application


A storage tank monitor

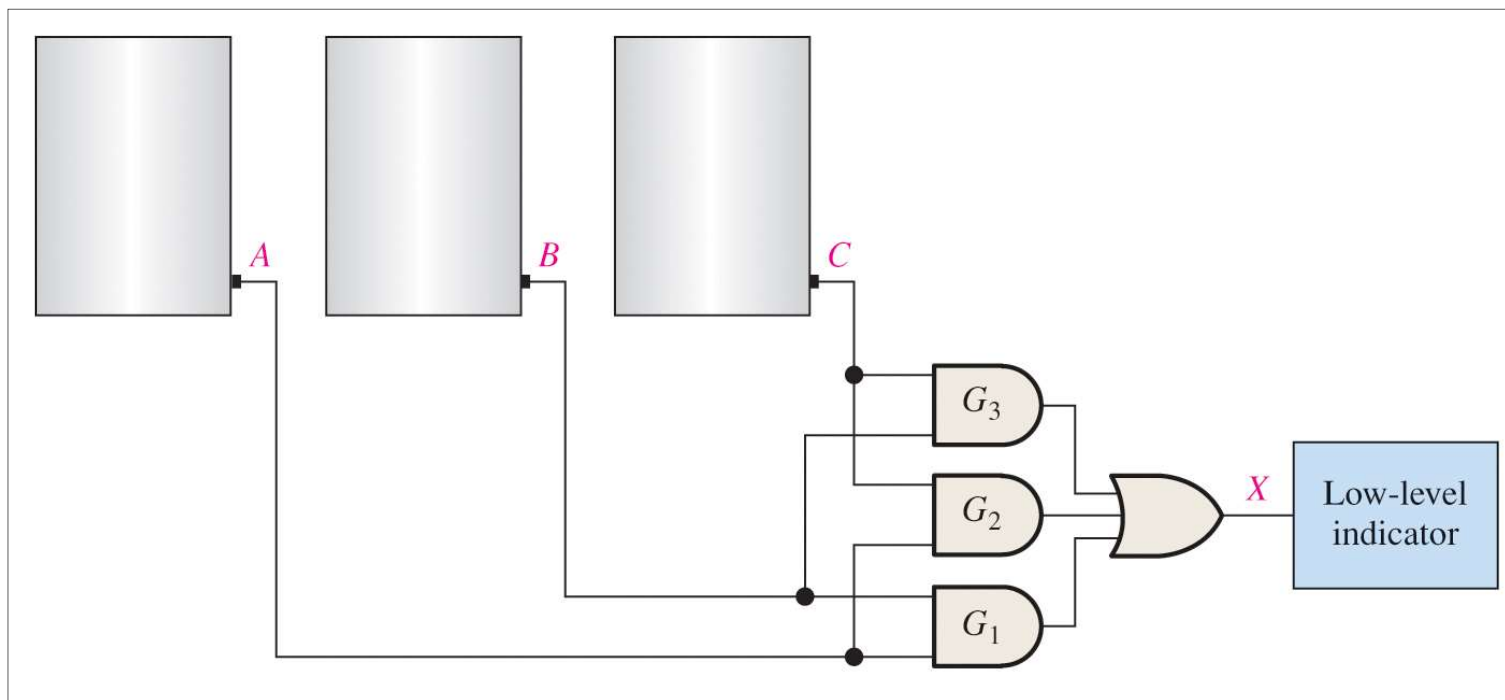

## Ch.5 Summary
 
# AND-OR-Invert Logic

When the output of a SOP form is inverted, the circuit is called an AND-OR-Invert circuit. The AOI configuration lends itself to product-of-sums (POS) implementation.



The output from an AND-OR-Invert logic circuit is LOW whenever A and B are HIGH, or C and D are HIGH.


## Exclusive-OR Logic

The truth table for an exclusive-OR gate is shown (right). Note that the output is HIGH whenever A and B are unequal.

The Boolean expression is  $X = \bar{A}B + A\bar{B}$

TABLE 4-2 • Truth table for an exclusive-OR.

A	B	X
0	0	0
0	1	1
1	0	1
1	1	0

 


## Exclusive-NOR Logic

The truth table for an exclusive-NOR gate is shown (right). Note that the output is HIGH whenever A and B are equal.

The Boolean expression is  $X = \overline{A}\overline{B} + AB$


TABLE 3-16 • Truth table for an exclusive-NOR gate.

INPUTS		OUTPUT
A	B	X
0	0	1
0	1	0
1	0	0
1	1	1

 

# An Exclusive-OR Logic Application
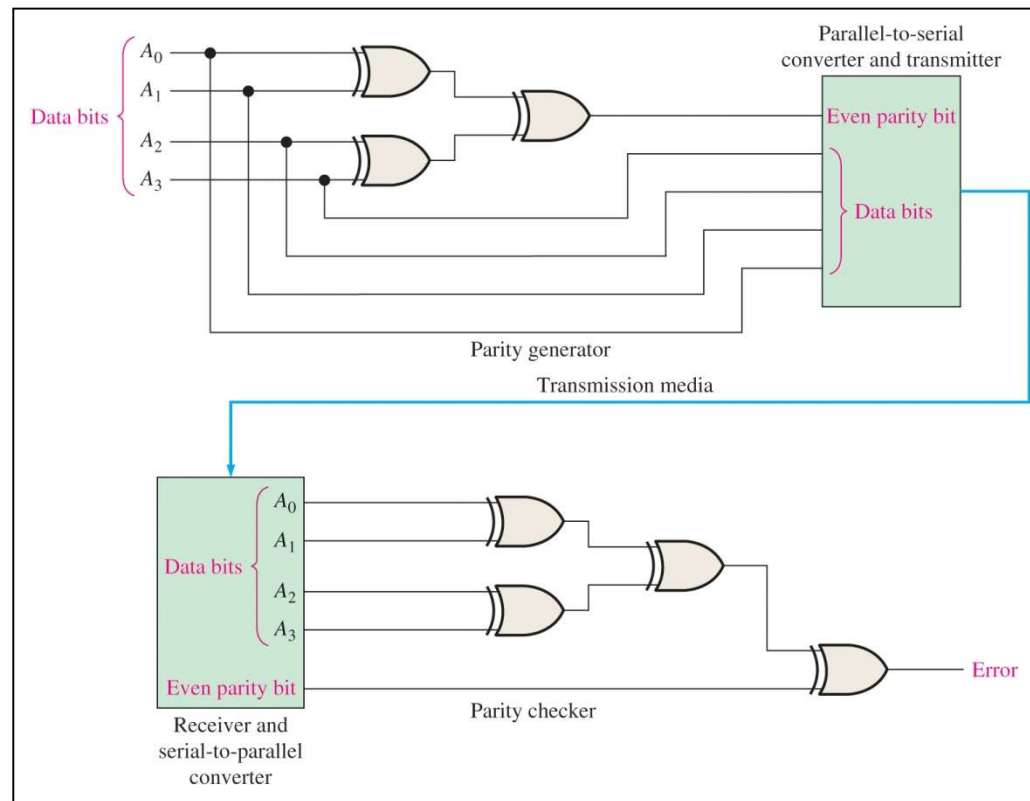
## Data transmission with error detection




## Ch.5 Summary

# Implementing Combinational Logic

Implementing a SOP expression is done by first forming the AND terms; then the terms are ORed together.

TABLE 4-3				
INPUTS			OUTPUT	PRODUCT TERM
A	B	C	X	
0	0	0	0	
0	0	1	0	
0	1	0	0	
0	1	1	1	$\bar{A}BC$
1	0	0	1	$A\bar{B}\bar{C}$
1	0	1	0	
1	1	0	0	
1	1	1	0	

 




## Ch.5 Summary

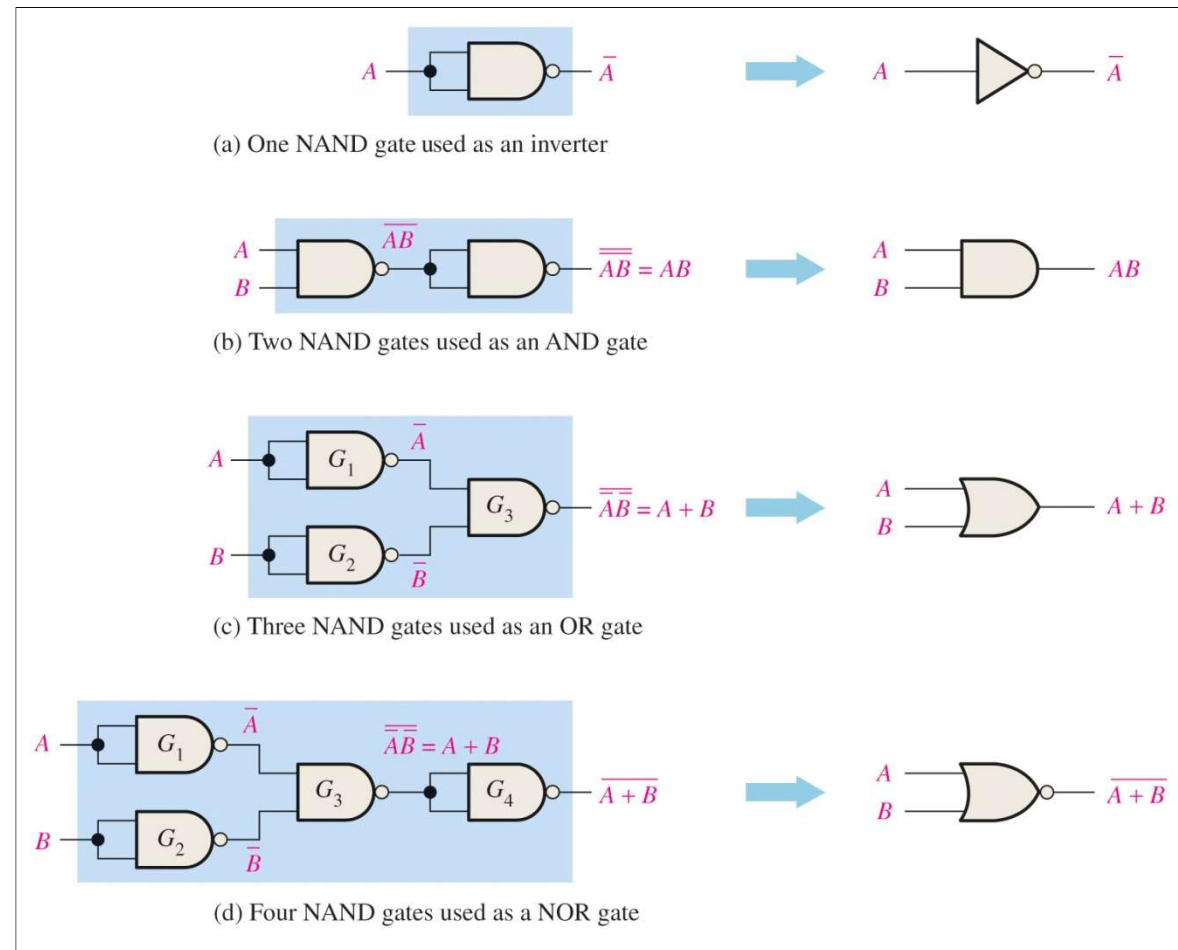
# Universal Gates

NAND gates are sometimes called **universal gates** because they can be used to produce the other basic Boolean functions.




## Ch.5 Summary

### NAND Logic for $AB+CD$

 


## Ch.5 Summary


# NAND Logic for $AB+CD$

 

 (a) Original NAND logic diagram showing effective gate operation relative to the output expression



 
(b) Equivalent NAND/Negative-OR logic diagram




(c) AND-OR equivalent

## Ch.5 Summary

# NAND Logic Diagram

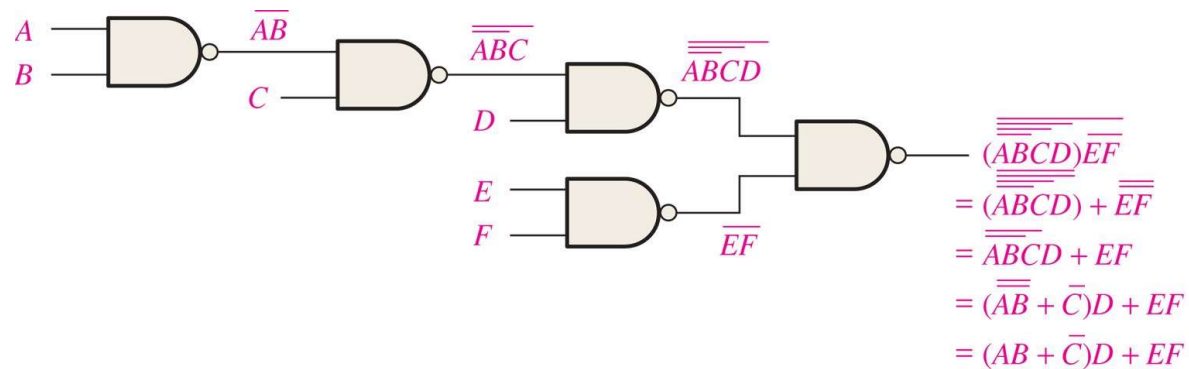

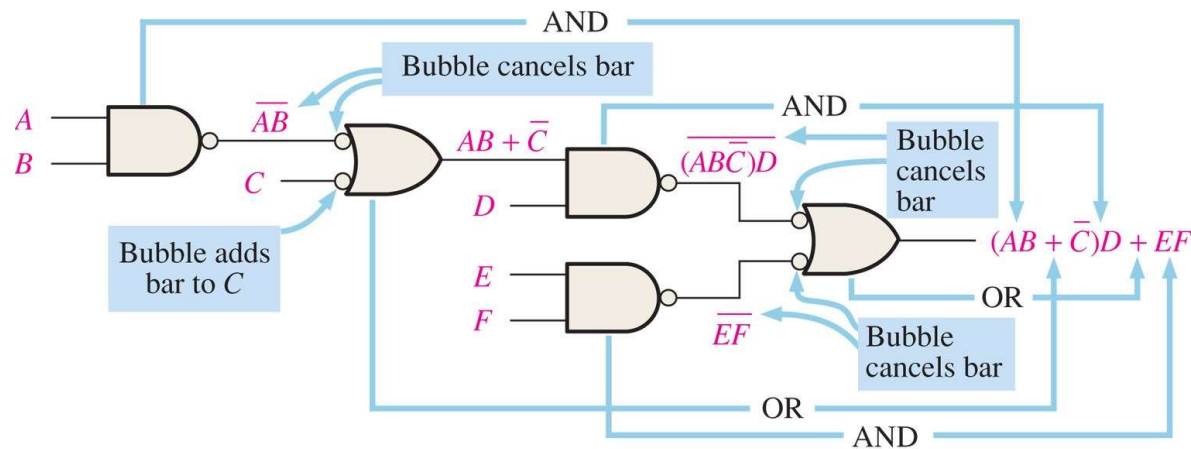(a) Several Boolean steps are required to arrive at final output expression.




(b) Output expression can be obtained directly from the function of each gate symbol in the diagram.

## Ch.5 Summary

 
# Universal Gates

NOR gates are also called **universal gates** because they can be used to produce the other basic Boolean functions.




## Ch.5 Summary

### NOR Logic for $(A+B)(C+D)$

 


## Ch.5 Summary

# NOR Logic for $(A+B)(C+D)$

 


(a)

 


(b)

## Ch.5 Summary

# NOR Logic Diagram

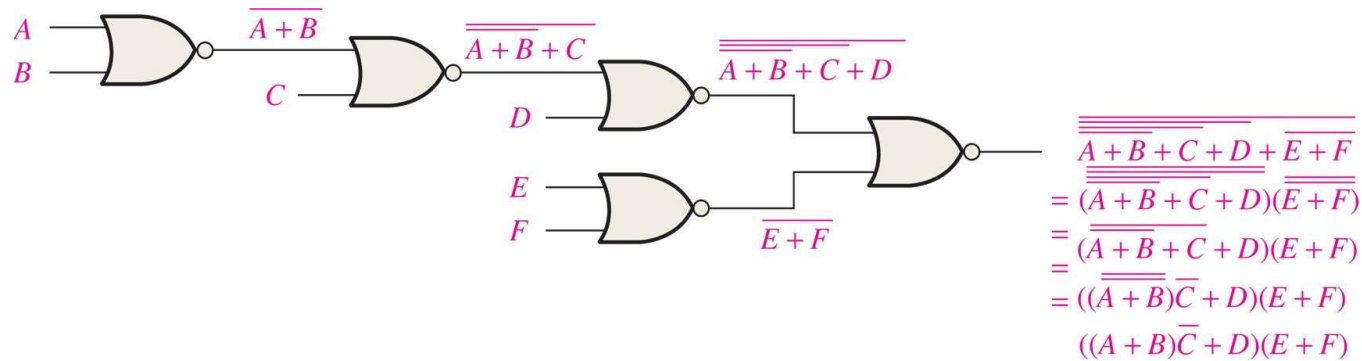

 (a) Final output expression is obtained after several Boolean steps.





(b) Output expression can be obtained directly from the function of each gate symbol in the diagram.





## Ch.5 Summary

# Pulse Waveform Operation

 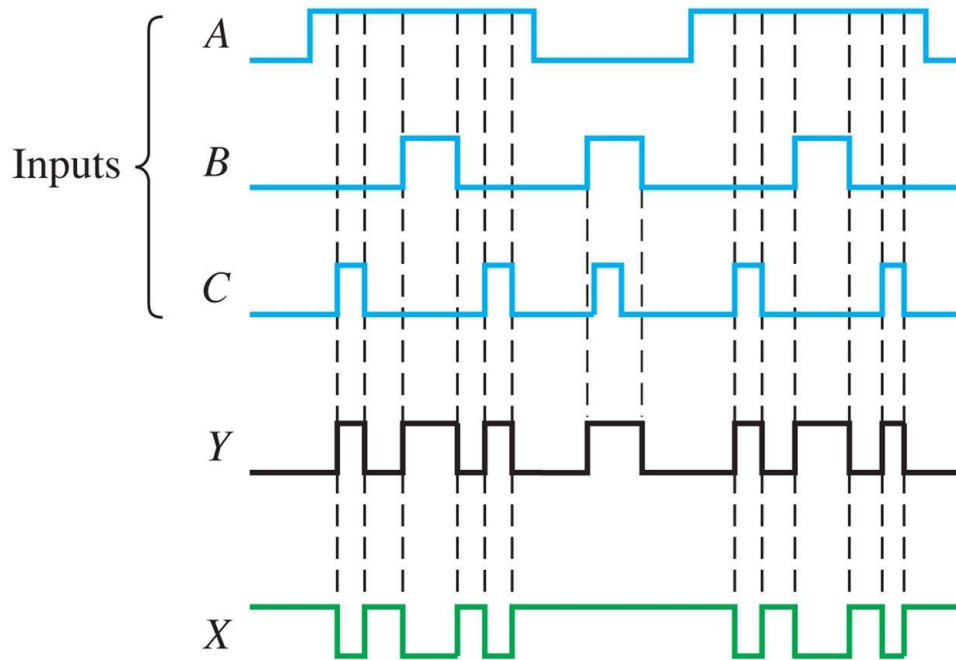

## Ch.5 Summary

# Pulse Waveform Operation

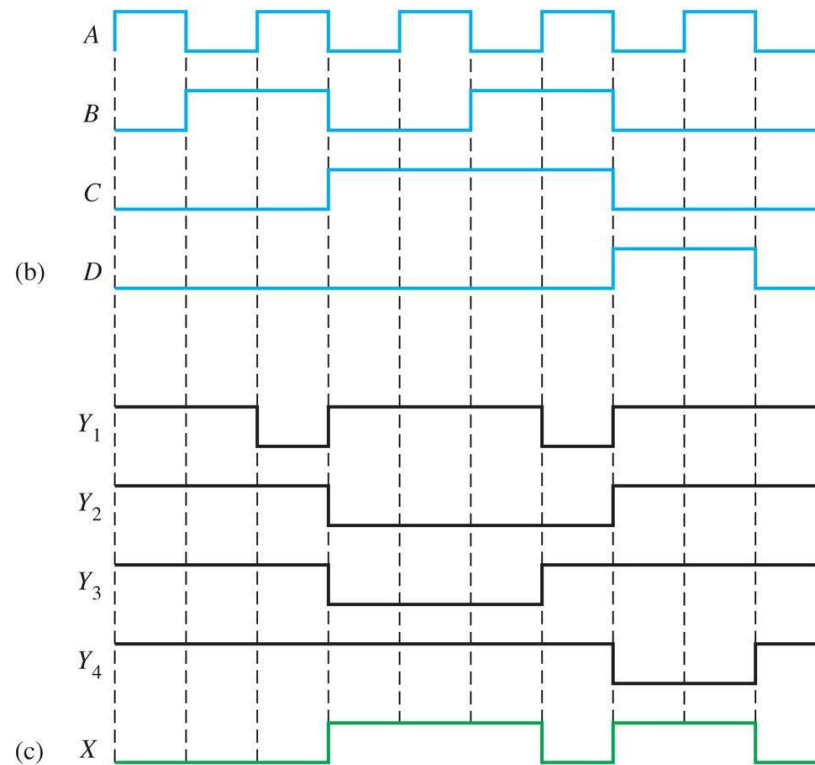 

## Ch.5 Summary

# Pulse Waveform Operation

