

Digital Fundamentals

Thomas L. Floyd

Logic Gates /
Boolean Algebra and Logic Simplification
Chapter 4

Ch.4 Summary

Boolean Variables

variable : 0 or 1.

complement : inverse of a variable

complement of A is \overline{A} .

literal : variable or its complement

Ch.4 Summary

Boolean Addition

Addition (Sum) : OR operation

Sum = 0 iff all of literals are 0

Sum = 1 iff any of literal is 1

Determine A , B , and C that satisfies $\overline{A} + B + \overline{C} = 0$

Each literal must equal 0; therefore $A = 1$, $B = 0$ and $C = 1$.

Ch.4 Summary

Boolean Multiplication

Multiplication : AND operation

Multiplication = 0 iff any of literal is 0

Multiplication = 1 iff all of literals are 1

Determine A , B and C if the product term of $\bar{A} \cdot \bar{B} \cdot C = 1$?

Each literal must = 1; therefore $A = 0$, $B = 0$ and $C = 1$.

Ch.4 Summary

Commutative Laws

The **commutative laws** apply to both addition and multiplication

In terms of the result, the order in which variables are ORed makes no difference.

$$A + B = B + A$$

For multiplication, the commutative law states:

In terms of the result, the order in which variables are ANDed makes no difference.

$$AB = BA$$

Ch.4 Summary

Associative Laws

The **associative laws** also apply to both addition and multiplication. For addition,

When ORing more than two variables, the result is the same regardless of the grouping of the variables.

$$A + (B + C) = (A + B) + C$$

For multiplication

When ANDing more than two variables, the result is the same regardless of the grouping of the variables.

$$A(BC) = (AB)C$$

How about NAND?


Ch.4 Summary

Distributive Law

The **distributive law** is the *factoring law*

$$AB + AC = A(B + C)$$

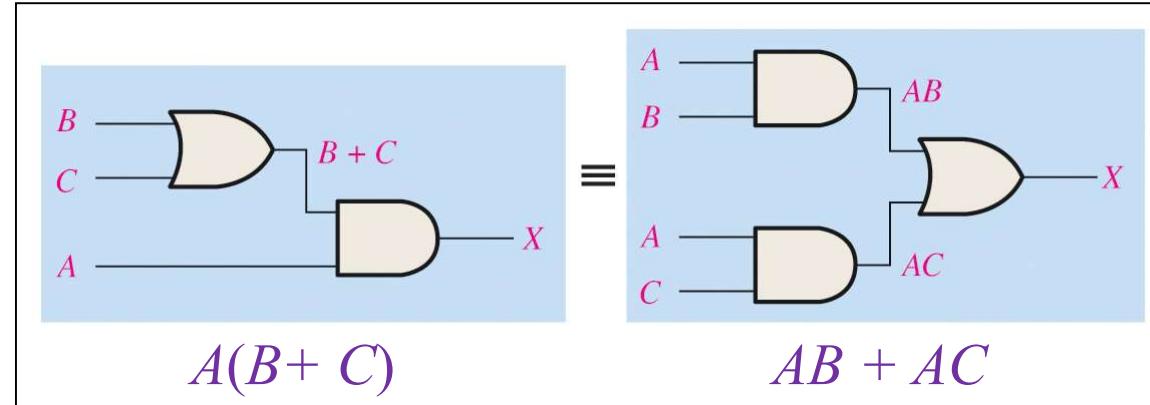The distributive law can be illustrated with equivalent circuits:



Ch.4 Summary

Rules of Boolean Algebra

$$1. A + 0 = A$$

$$2. A + 1 = 1$$

$$3. A \cdot 0 = 0$$

$$4. A \cdot 1 = A$$

$$5. A + A = A$$

$$6. A + \bar{A} = 1$$

$$7. A \cdot A = A$$

$$8. A \cdot \bar{A} = 0$$

$$9. \bar{\bar{A}} = A$$

$$10. A + AB = A$$

$$11. A + \bar{A}B = A + B$$

$$12. (A + B)(A + C) = A + BC$$

Ch.4 Summary


Rules of Boolean Algebra

Rule 1: $A + 0 = A$

When $A = 1$, the input causes the output to go to $X = 1$.

When $A = 0$, the 0 inputs cause the output to go to $X = 0$.

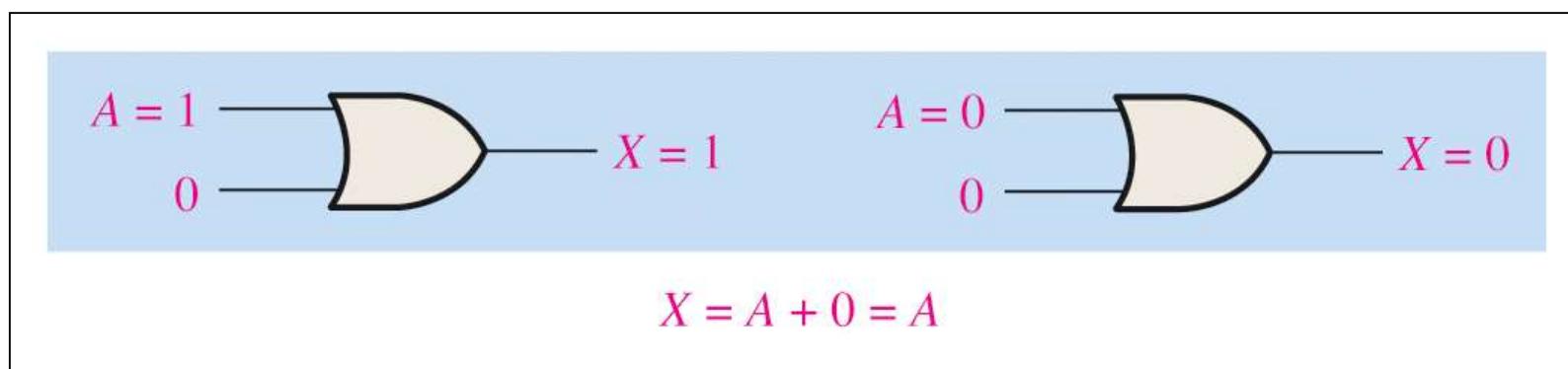In either case, the value of X equals the value of A .




Ch.4 Summary

Rules of Boolean Algebra

Rule 2: $A + 1 = 1$

When $A = 1$, the inputs cause the output to go to $X = 1$.

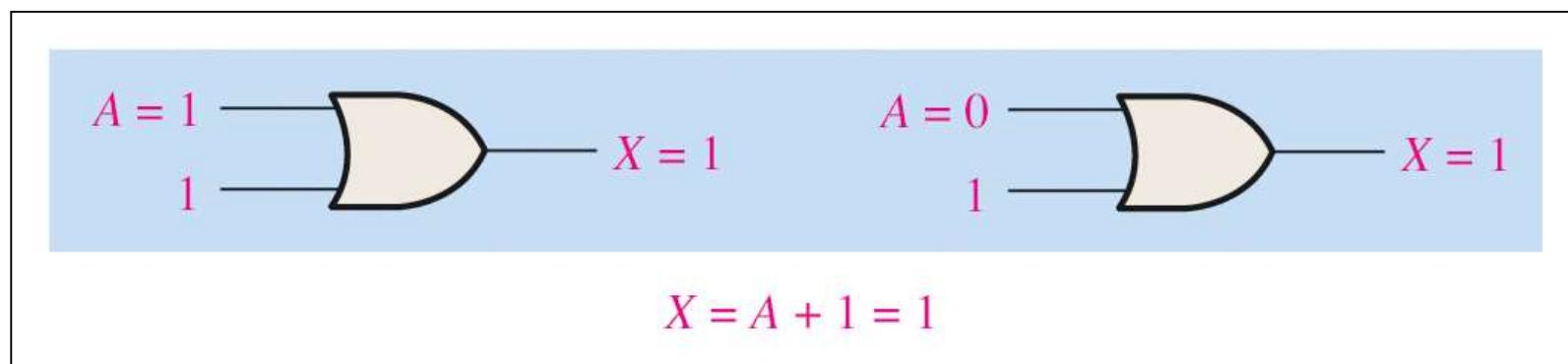When $A = 0$, the 1 input caused the output to go to $X = 1$.
In either case, the value of X equals one (1).




Ch.4 Summary

Rules of Boolean Algebra

Rule 3: $A \cdot 0 = 0$

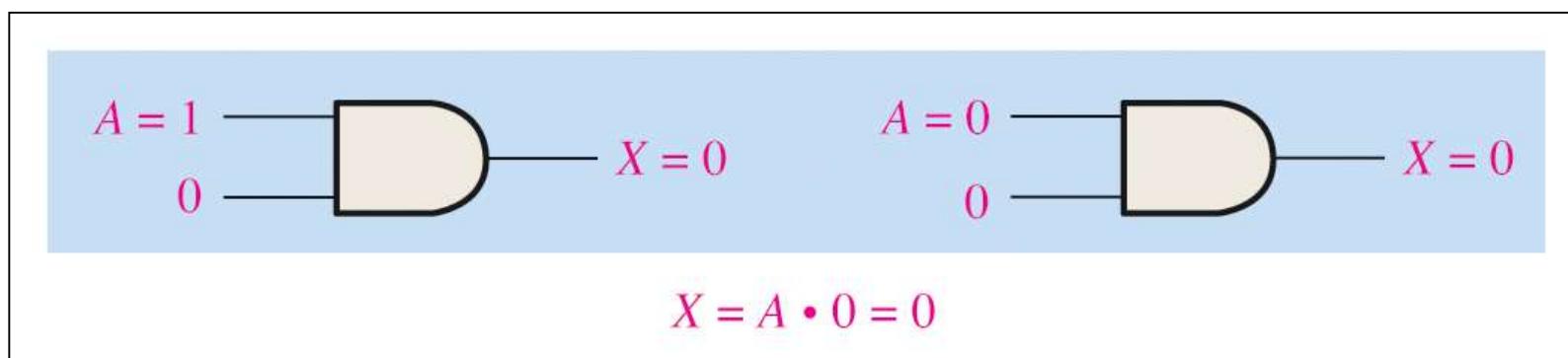When either input to an AND gate equals 0, the output from the gate has a value of $X = 0$, regardless of the value at the other input.




Ch.4 Summary

Rules of Boolean Algebra

Rule 4: $A \bullet 1 = A$

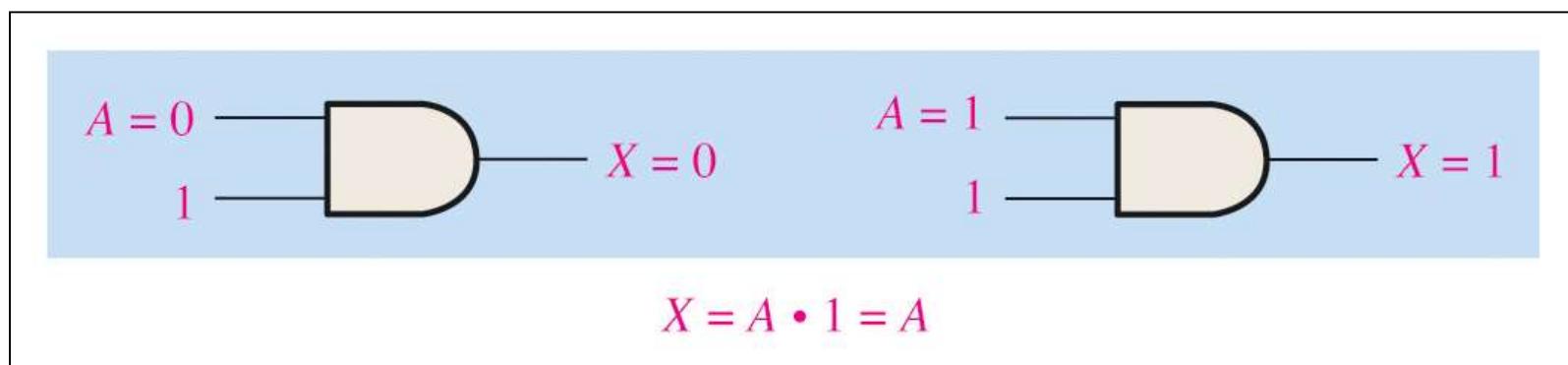When one input to an AND gate equals 1, the output from the gate has a value of $X = A$. As shown, $X = 1$ when $A = 1$ and $X = 0$ when $A = 0$.




Ch.4 Summary

Rules of Boolean Algebra

Rule 5: $A + A = A$

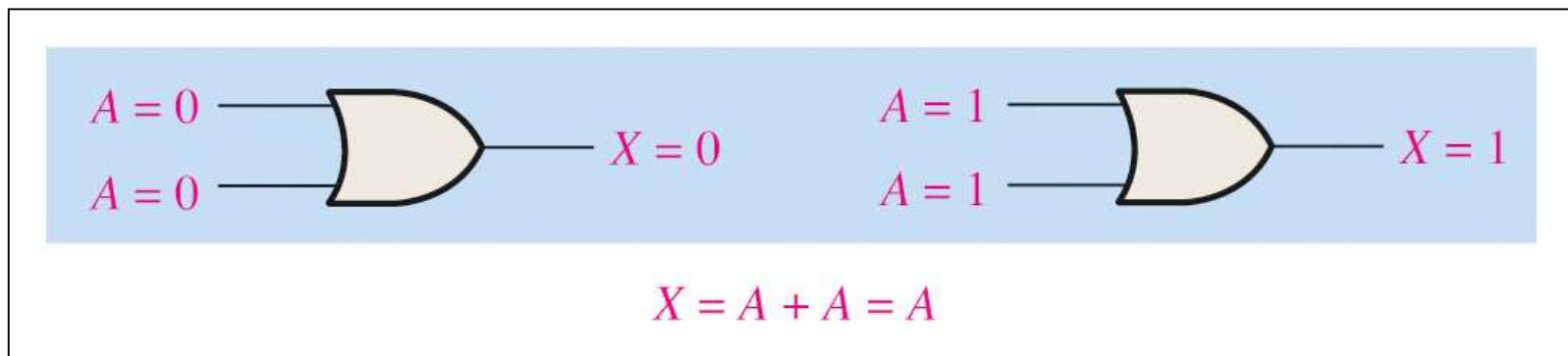When the inputs to an OR gate are equal, the output equals the value at the inputs. When both inputs equal 1, the gate output is $X = 1$. When both inputs equal 0, the gate output is $X = 0$.




Ch.4 Summary

Rules of Boolean Algebra

Rule 6: $A + \bar{A} = 1$

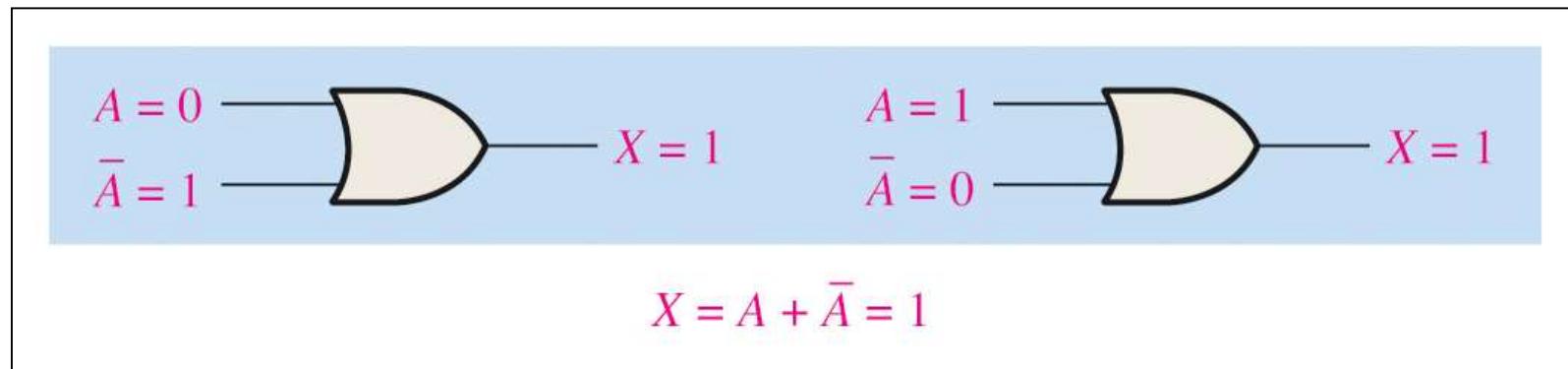When the inputs to an OR gate are unequal (complements), one of the two always equals 1. When either input equals 1, the gate output is $X = 1$. Therefore, the output from the OR gate equals 1 whenever the inputs are unequal (complementary).




Ch.4 Summary

Rules of Boolean Algebra

Rule 7: $A \cdot A = A$

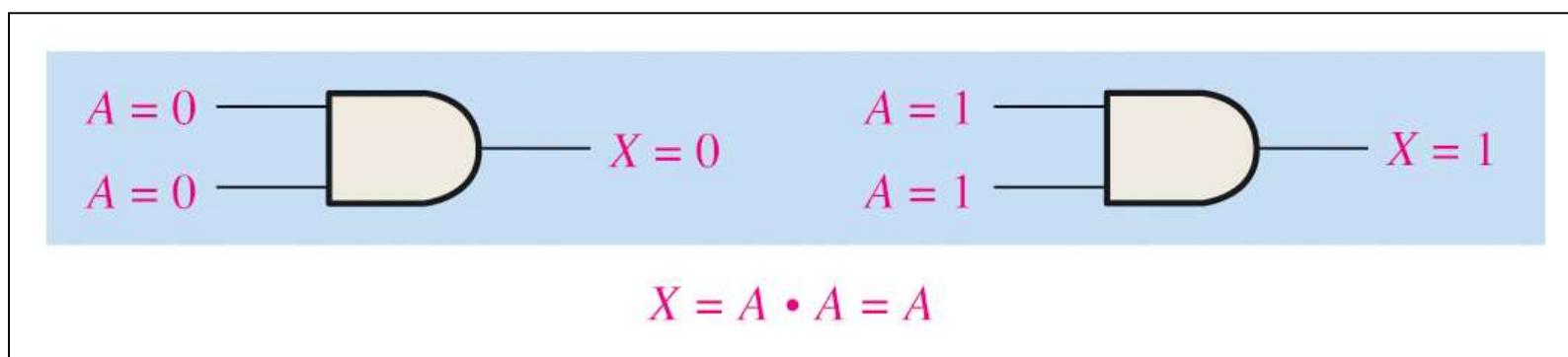When the inputs to an AND gate are equal, the gate output also equals that value. Thus, $X = 1$ when both inputs equal 1 and $X = 0$ when both inputs equal 0.




Ch.4 Summary

Rules of Boolean Algebra

Rule 8: $A \cdot \bar{A} = 0$

When the inputs to an AND gate are unequal (complements), one of the two always equals 0.

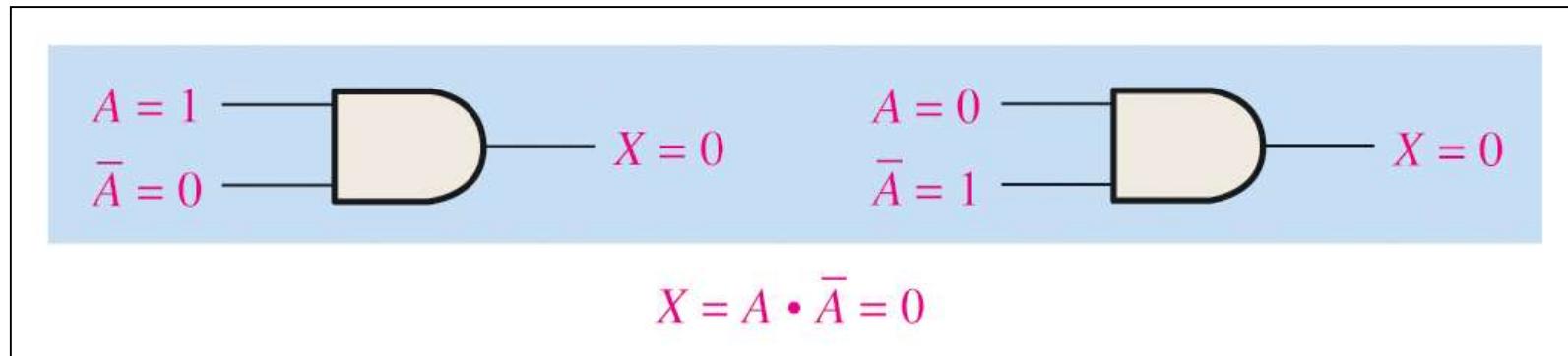When either input equals 0, the gate output is $X = 0$.
Therefore, the output from the AND gate equals 0 whenever the inputs are unequal (complementary).




Ch.4 Summary

Rules of Boolean Algebra

Rule 9: $\overline{\overline{A}} = A$

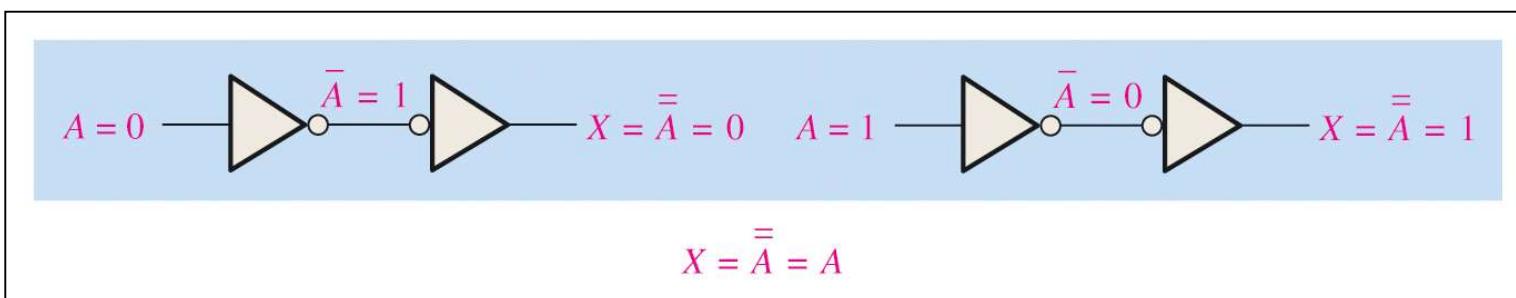When a value is inverted, it is the complement of the original value. When inverted a second time, it returns to its original value. Thus, $A = 0$ inverted twice equals 0 and $A = 1$ inverted twice equals 1.



Ch.4 Summary

Rules of Boolean Algebra

Rule 10: $A + AB = A$

The circuit and truth table (below) can be used to demonstrate this rule. The truth table shows the outputs from the circuit for every possible combination of A and B. In each case, the output from the OR gate equals the value of A. Thus, $A + AB$ always equals the value of A.

A	B	AB	$A + AB$
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1

↑ ↑

equal

Ch.4 Summary



Rules of Boolean Algebra

Rule 11: $A + \bar{A}B = A + B$

The circuits and truth table (below) demonstrate this rule. The truth table shows the outputs from the two circuits are equal for every possible combination of A and B . As such, the two functions ($A + \bar{A}B$) and ($A + B$) are equal.

A	B	$\bar{A}B$	$A + \bar{A}B$	$A + B$
0	0	0	0	0
0	1	1	1	1
1	0	0	1	1
1	1	0	1	1

↑ equal ↑

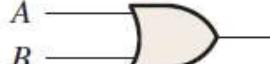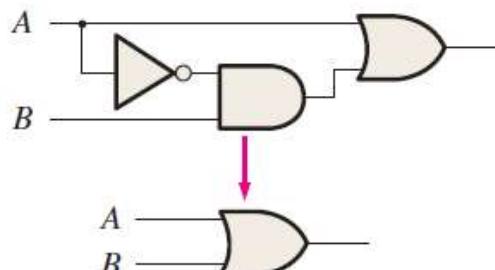

Ch.4 Summary


Rules of Boolean Algebra

Rule 12: $(A + B)(A + C) = A + BC$

The circuits and truth table (below) demonstrate this rule. The truth table shows the outputs from the two circuits are equal for every possible combination of A and B . As such, the two functions $(A + B)(A + C)$ and $A + BC$ are equal.

A	B	C	$A + B$	$A + C$	$(A + B)(A + C)$	BC	$A + BC$
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	1	1	1	1
1	0	0	1	1	1	0	1
1	0	1	1	1	1	0	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

↑ ↓ equal ↑

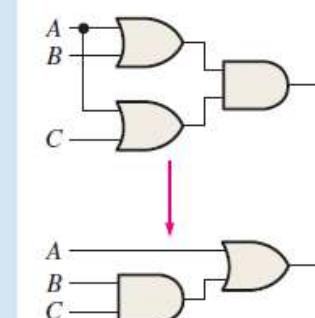


Ch.4 Summary

DeMorgan's Theorem

The complement of two or more ANDed variables equals the OR of the individual variable complements.
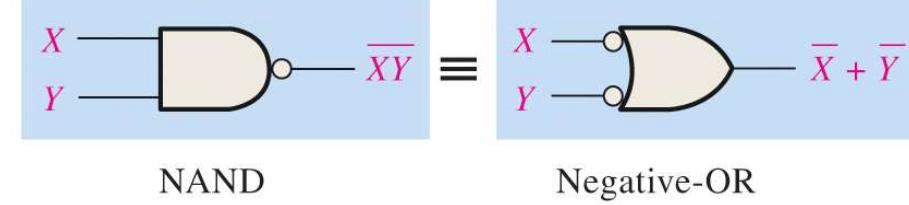
$$\overline{XY} = \overline{X} + \overline{Y}$$




INPUTS		OUTPUT	
X	Y	\overline{XY}	$\overline{X} + \overline{Y}$
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0

Ch.4 Summary

DeMorgan's Theorem

The complement of two or more ORed variables equals the AND of the individual variable complements.
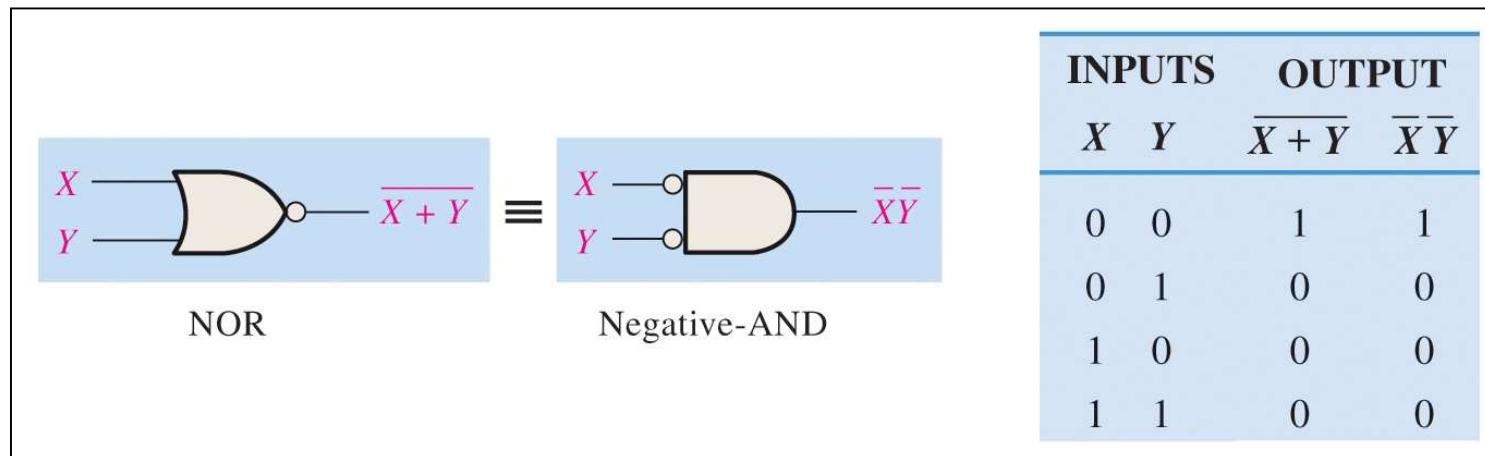
$$\overline{X + Y} = \overline{X} \cdot \overline{Y}$$



Ch.4 Summary

DeMorgan's Theorem

The complement of two or more ORed variables equals the AND of the individual variable complements.

$$\overline{X + Y + Z} = \overline{X} \cdot \overline{Y} \cdot \overline{Z}$$

$$\overline{X \cdot Y \cdot Z} = \overline{X} + \overline{Y} + \overline{Z}$$

Ch.4 Summary

DeMorgan's Theorem: Application


$$\overline{A + \overline{B}\overline{C}} + D(\overline{E} + \overline{\overline{F}}) = ?$$

$$\overline{(AB + C)(A + BC)} = ?$$

Ch.4 Summary

Boolean Expression for a Logic Circuit

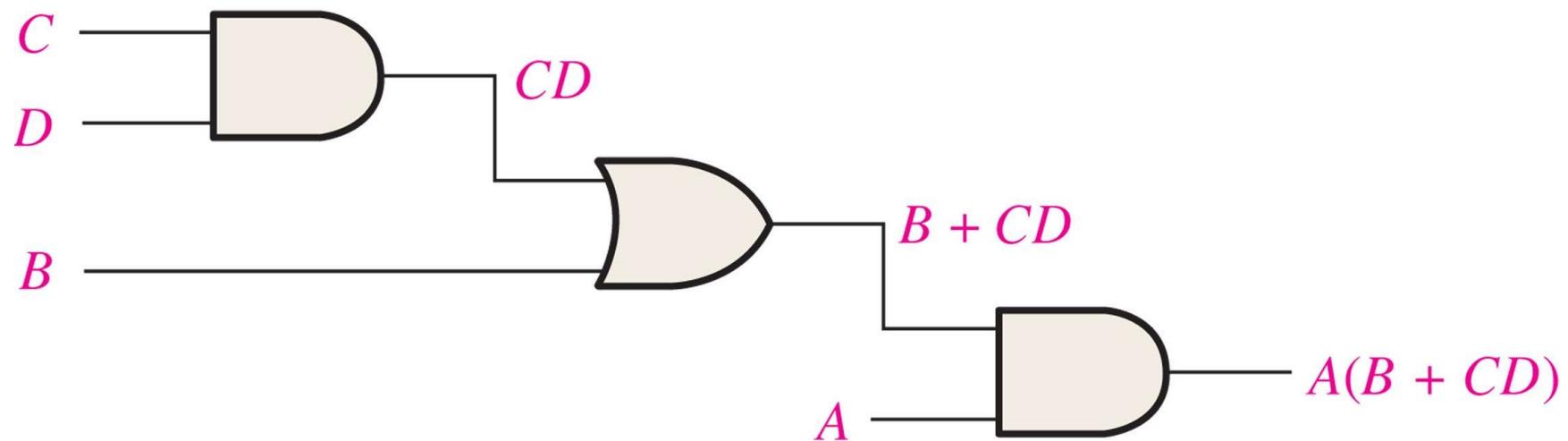Derive Boolean expression for a given combinatorial logic circuit.



Ch.4 Summary

Constructing a Truth Table

TABLE 4–5


Truth table for the logic circuit in Figure 4–18.

Inputs				Output
<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	$A(B + CD)$
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

Ch.4 Summary

Logic Simplification

$$AB + A(B+C) + B(B+C) = B + AC$$

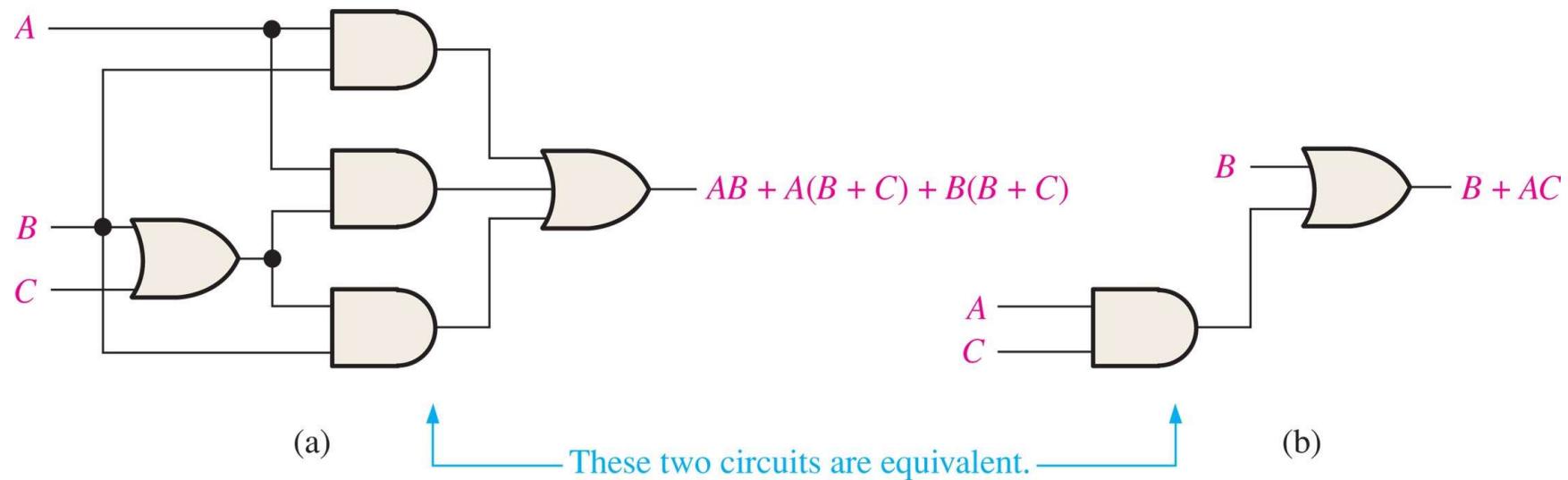

Ch.4 Summary

Logic Simplification

$$(\bar{A} + B)C + ABC = ?$$

Ch.4 Summary

Sum-of-Products (SOP) Form

Two or more product terms are summed by Boolean addition

$$AB + BCD + AC \quad \checkmark$$


$$\bar{A}B + \bar{A}B\bar{C} + AC \quad \checkmark$$

$$\bar{A}B + \overline{ABC} + AC \quad \times$$

Ch.4 Summary

Sum-of-Products (SOP) Form


$$AB + BCD + AC$$

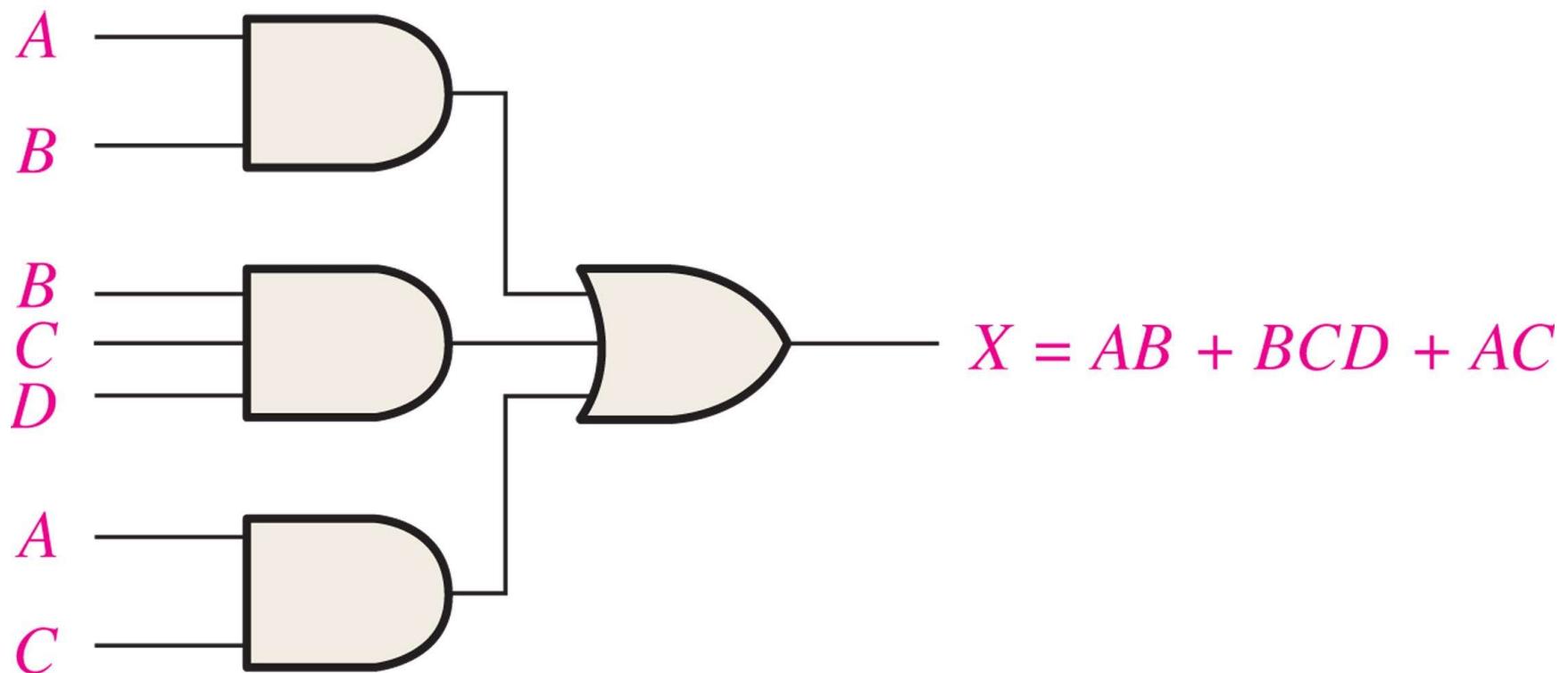

Ch.4 Summary

Sum-of-Products (SOP) Form

$$AB + BCD + AC$$

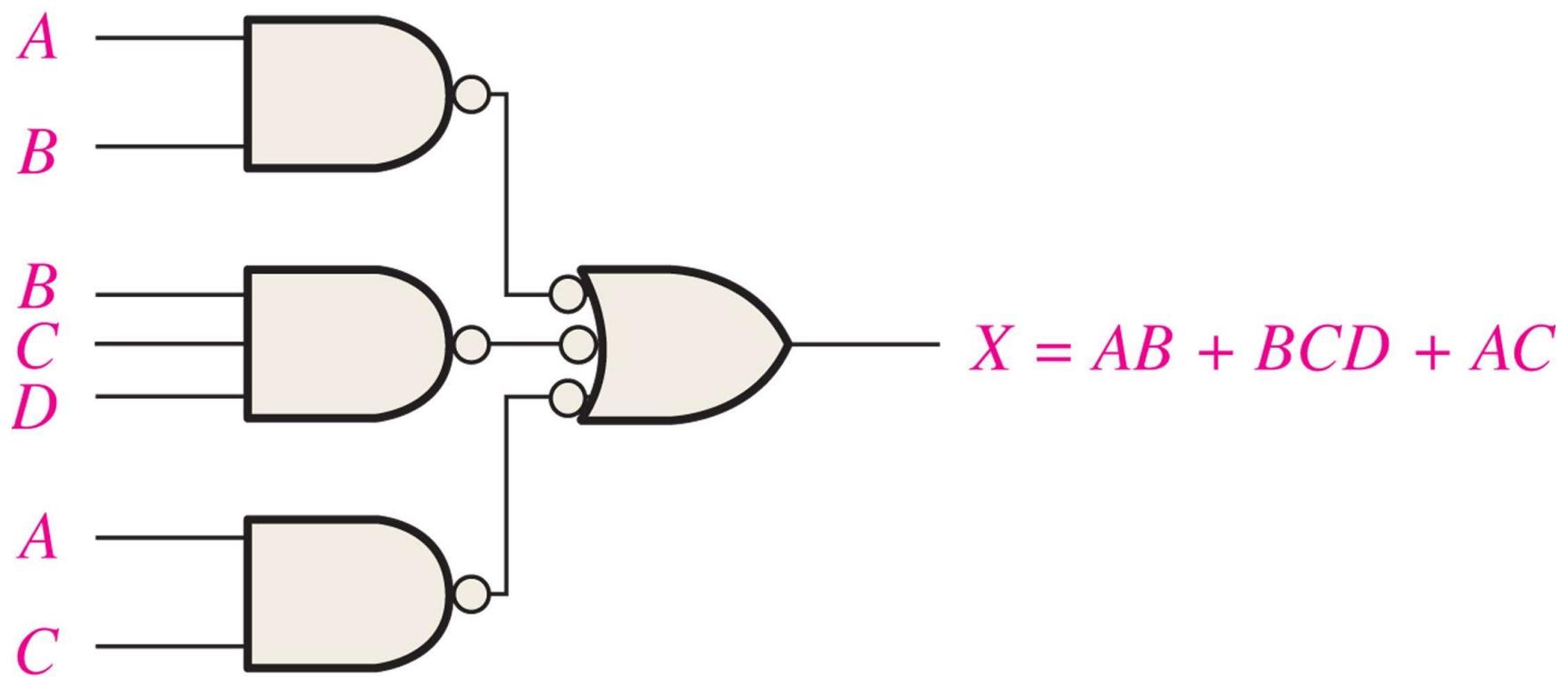

Ch.4 Summary

Standard SOP

All the variables in the domain appear in each product term in the expression (use $D + \bar{D} = 1$)

$$A\bar{B}C + \bar{A}\bar{B} + AB\bar{C}D$$



$$\begin{aligned} & A\bar{B}CD + A\bar{B}C\bar{D} + \bar{A}\bar{B}CD \\ & + \bar{A}\bar{B}C\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}\bar{C}\bar{D} + AB\bar{C}D \end{aligned}$$

Ch.4 Summary

Binary Representation

SOP expression is equal to 1 only if one or more of the product terms in the expression is equal to 1

$$ABCD \rightarrow 1 \cdot 1 \cdot 1 \cdot 1$$

$$A\bar{B}\bar{C}D \rightarrow 1 \cdot \bar{0} \cdot \bar{0} \cdot 1$$

$$\bar{A}\bar{B}\bar{C}\bar{D} \rightarrow \bar{0} \cdot \bar{0} \cdot \bar{0} \cdot \bar{0}$$

Ch.4 Summary

SOP to Truth Table

TABLE 4-6

Inputs			Output	Product Term
A	B	C	X	
0	0	0	0	
0	0	1	1	$\overline{A} \overline{B} C$
0	1	0	0	
0	1	1	0	
1	0	0	1	$A \overline{B} \overline{C}$
1	0	1	0	
1	1	0	0	
1	1	1	1	ABC

Ch.4 Summary

Product-of-Sums (POS) Form

Two or more product terms are summed by Boolean addition

$$(\bar{A}+B)(A+\bar{B}+C) \quad \checkmark$$


$$(A+B)(A+\bar{B}+C)(\bar{A}+C) \quad \checkmark$$

$$(A+B)(\bar{A}+\bar{B}+\bar{C})(\bar{A}+C) \quad \times$$

Ch.4 Summary

Product-of-Sums (POS) Form

$$(A + B)(B + C + D)(A + C)$$

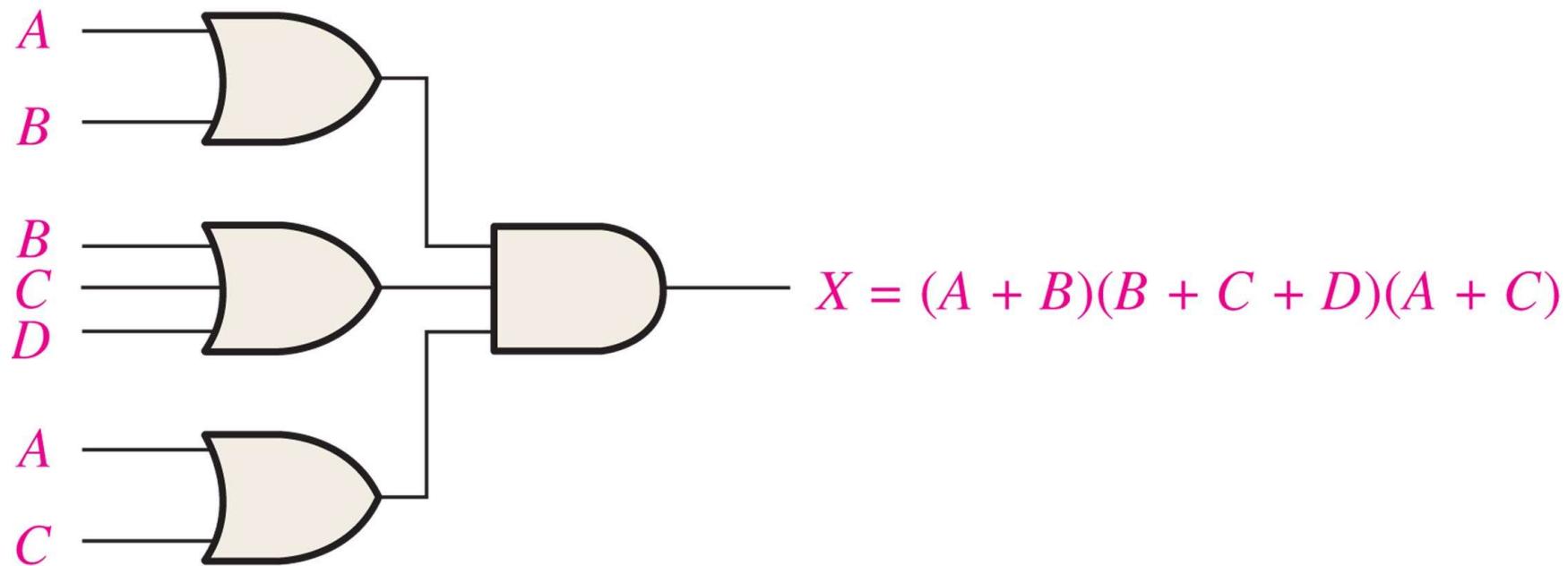

Ch.4 Summary

Standard POS

All the variables in the domain appear in each sum term
in the expression

(use $D\bar{D} = 0$ and $A + BC = (A + B)(A + C)$)

$$(A + \bar{B} + C)(A + B + \bar{D})$$



$$(A + \bar{B} + C + D)(A + \bar{B} + C + \bar{D})$$

$$(A + B + C + \bar{D})(A + B + \bar{C} + \bar{D})$$

Ch.4 Summary

Binary Representation

POS expression is equal to 0 only if one or more of the sum terms in the expression is equal to 0

$$A + B + C + D \rightarrow 0 + 0 + 0 + 0$$

$$A + \bar{B} + \bar{C} + D \rightarrow 0 + \bar{1} + \bar{1} + 0$$

$$\bar{A} + \bar{B} + \bar{C} + \bar{D} \rightarrow \bar{1} + \bar{1} + \bar{1} + \bar{1}$$

Ch.4 Summary

POS to Truth Table

TABLE 4-7

Inputs			Output	Sum Term
A	B	C	X	
0	0	0	0	$(A + B + C)$
0	0	1	1	
0	1	0	0	$(A + \bar{B} + C)$
0	1	1	0	$(A + \bar{B} + \bar{C})$
1	0	0	1	
1	0	1	0	$(\bar{A} + B + \bar{C})$
1	1	0	0	$(\bar{A} + \bar{B} + C)$
1	1	1	1	

Ch.4 Summary

SOP to Truth Table

TABLE 4-6

Inputs			Output	Product Term
A	B	C	X	
0	0	0	0	
0	0	1	1	$\overline{A} \overline{B} C$
0	1	0	0	
0	1	1	0	
1	0	0	1	$A \overline{B} \overline{C}$
1	0	1	0	
1	1	0	0	
1	1	1	1	ABC

Ch.4 Summary

Karnaugh Map

Karnaugh map provides a systematic method for simplifying Boolean expressions.

Karnaugh map is similar to a truth table.

	$AB \backslash C$	0	1
00			
01			
11			
10			


(a)

	$AB \backslash C$	0	1
00	$\bar{A}\bar{B}\bar{C}$	$\bar{A}\bar{B}C$	
01	$\bar{A}B\bar{C}$	$\bar{A}BC$	
11	ABC	$A\bar{B}C$	
10	$A\bar{B}\bar{C}$	$A\bar{B}C$	


(b)

Ch.4 Summary

4-Variable Karnaugh Map

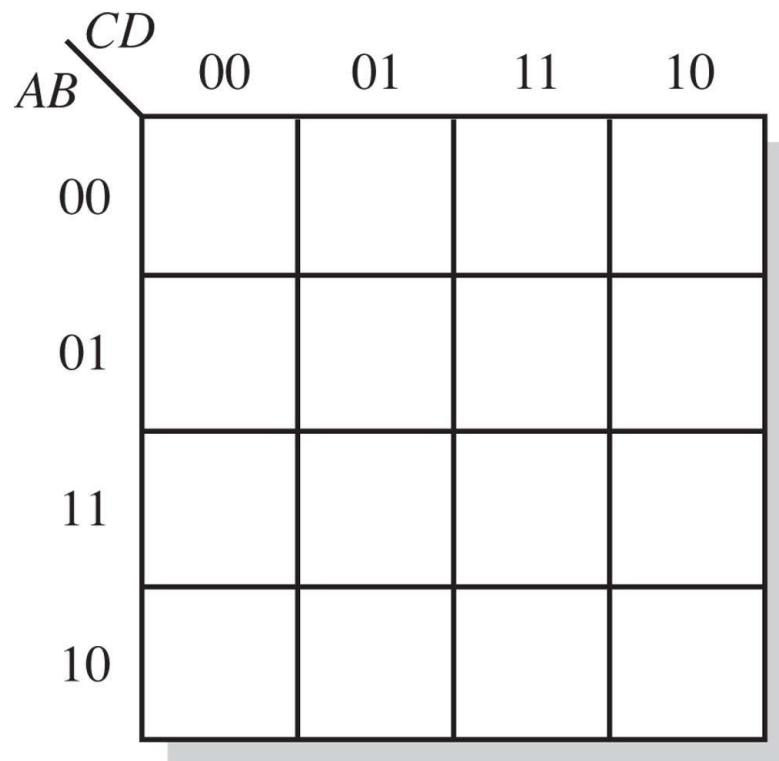


(a)

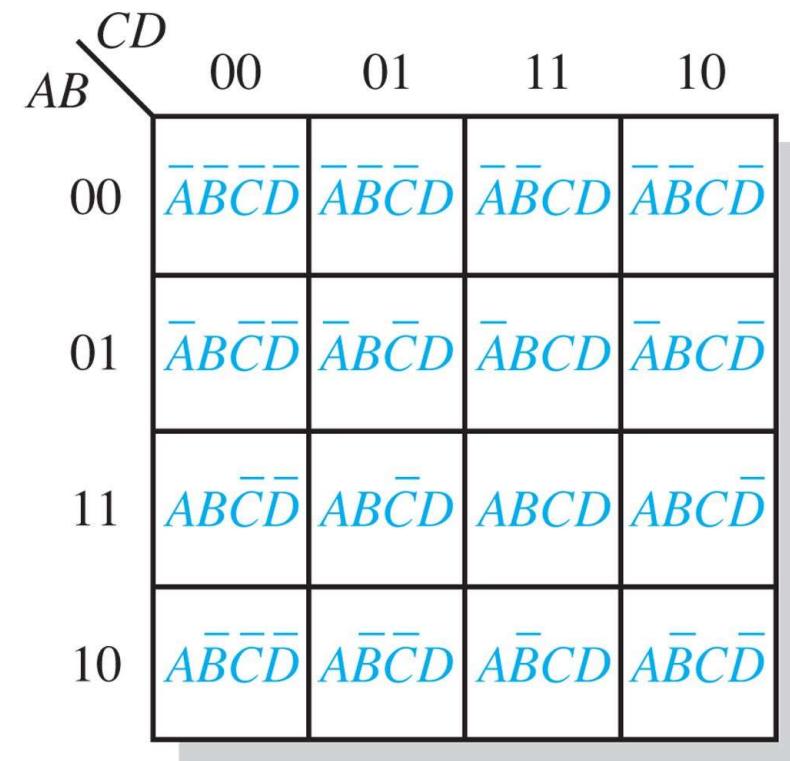

(b)


Ch.4 Summary

4-Variable Karnaugh Map

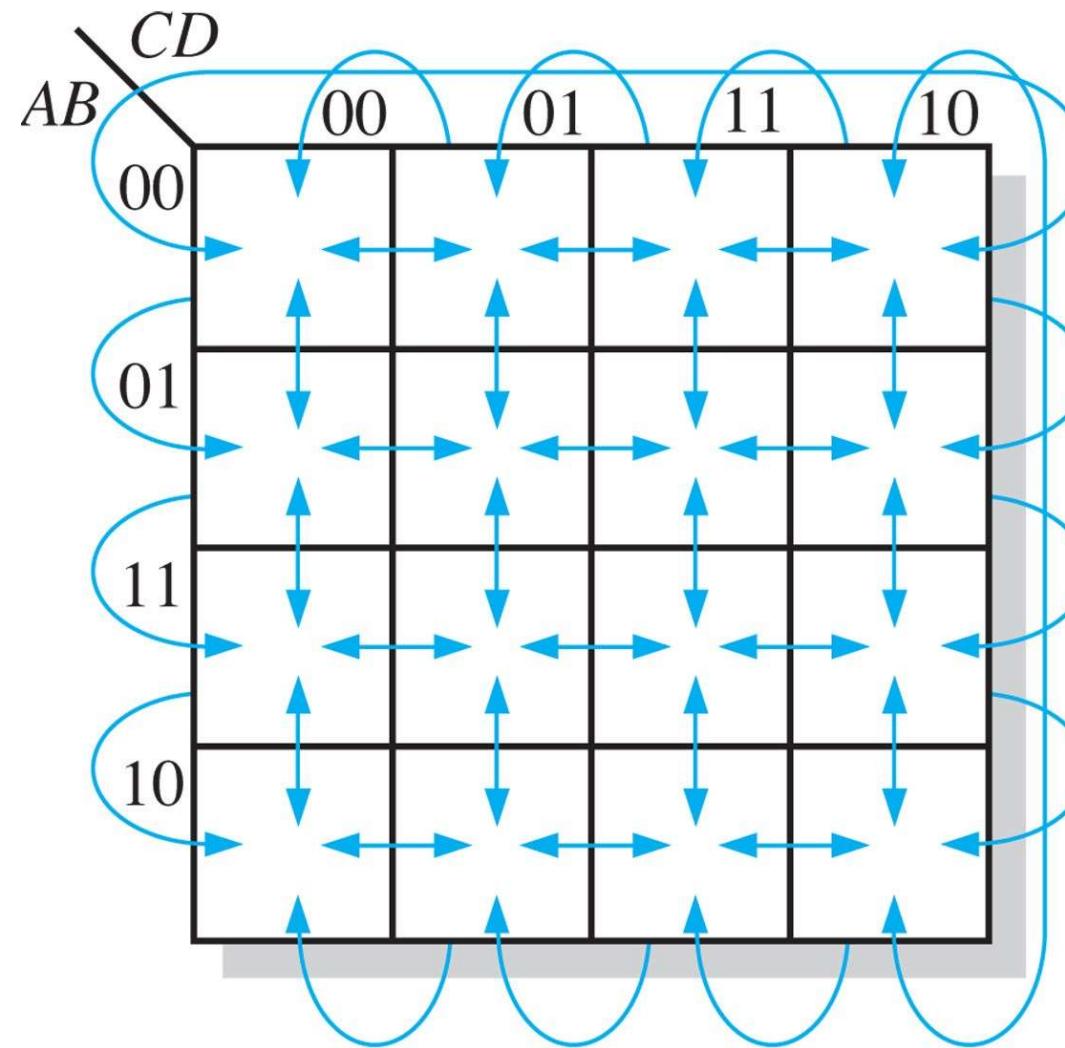

Ch.4 Summary


Mapping a Standard SOP

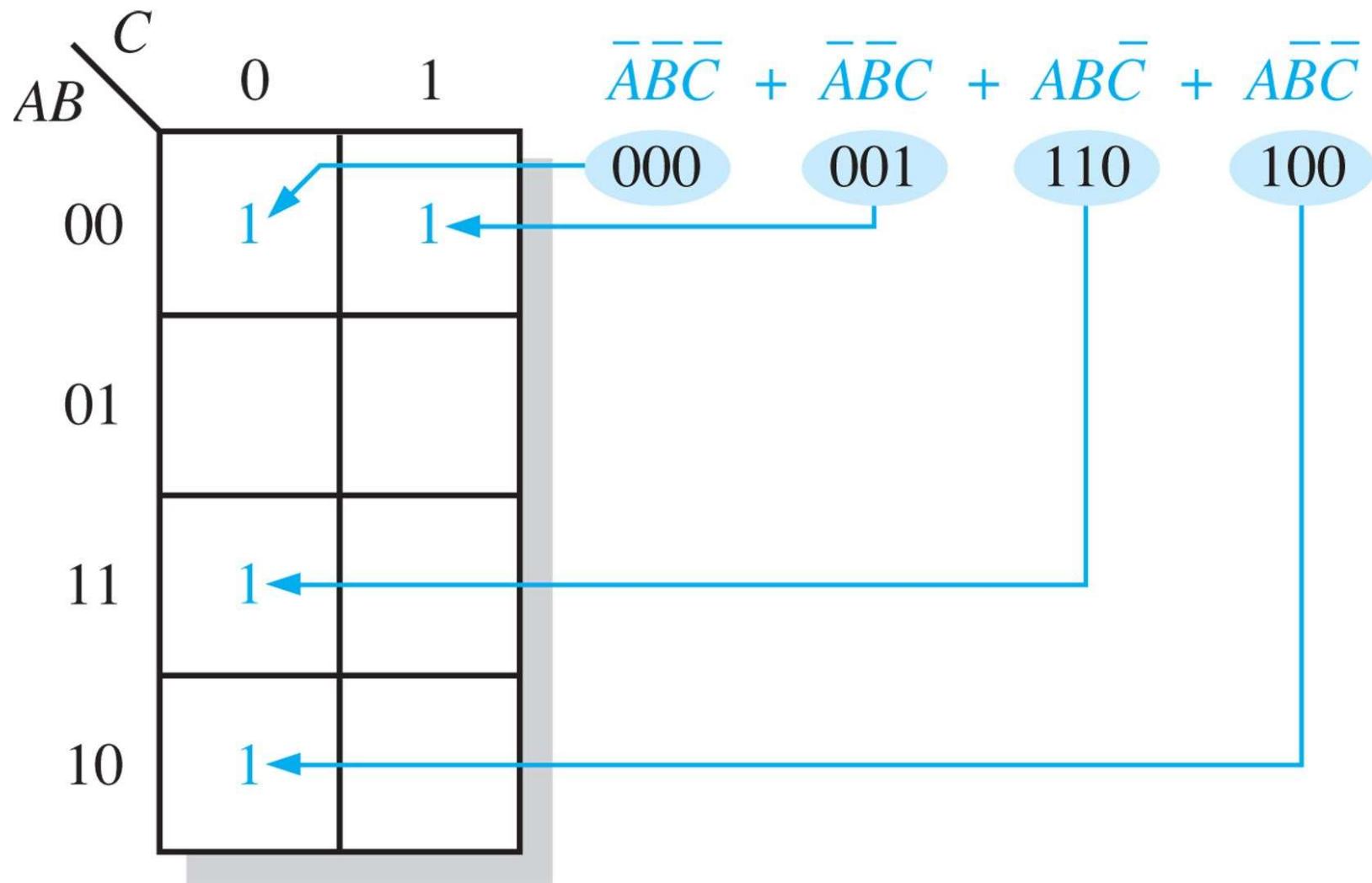

Ch.4 Summary

Mapping a Standard SOP
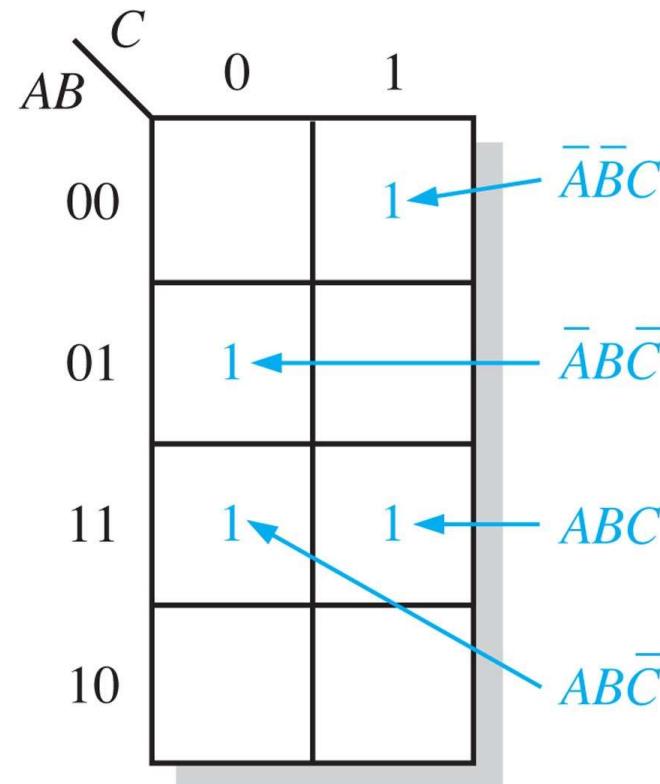
$$\bar{A}\bar{B}C + \bar{A}B\bar{C} + AB\bar{C} + ABC$$




Ch.4 Summary

Mapping from Truth Table

$$X = \overline{ABC} + \overline{A}\overline{B}\overline{C} + A\overline{B}\overline{C} + ABC$$


Inputs			Output
A	B	C	X
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

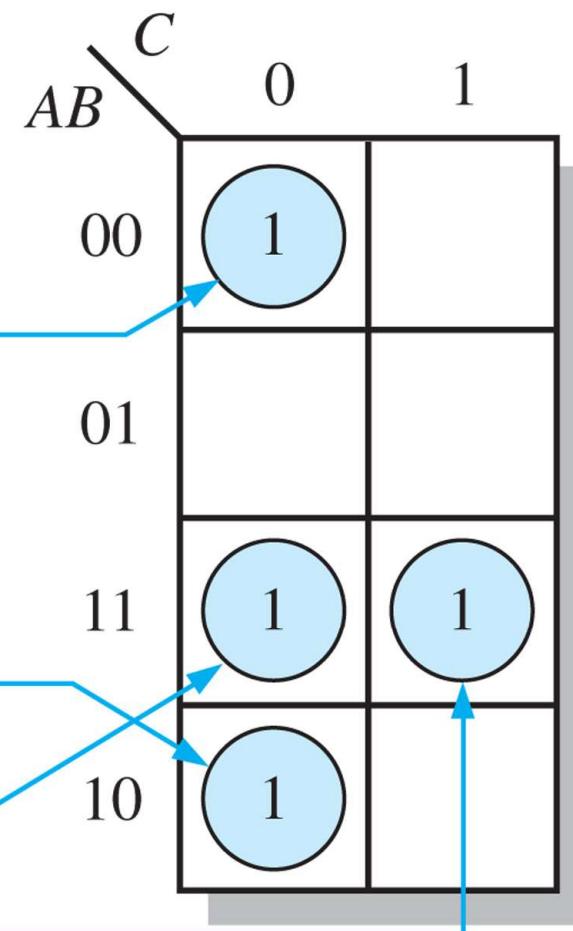

Ch.4 Summary

Mapping a SOP


$$\bar{A} + A\bar{B} + AB\bar{C}$$

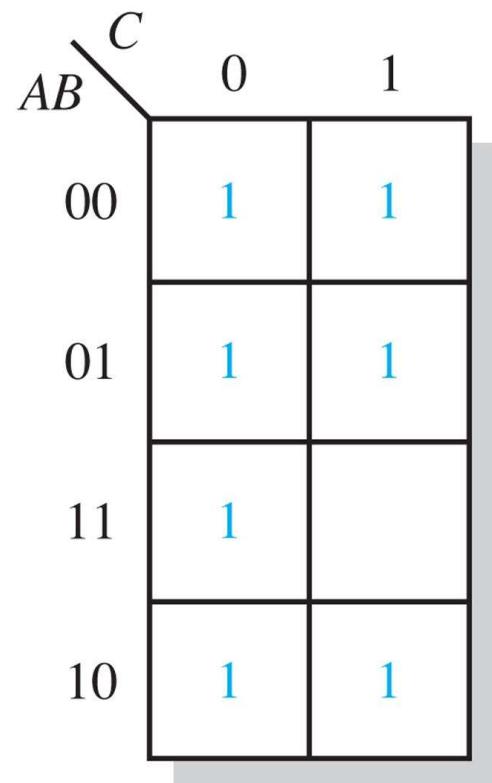

Ch.4 Summary


Mapping a SOP
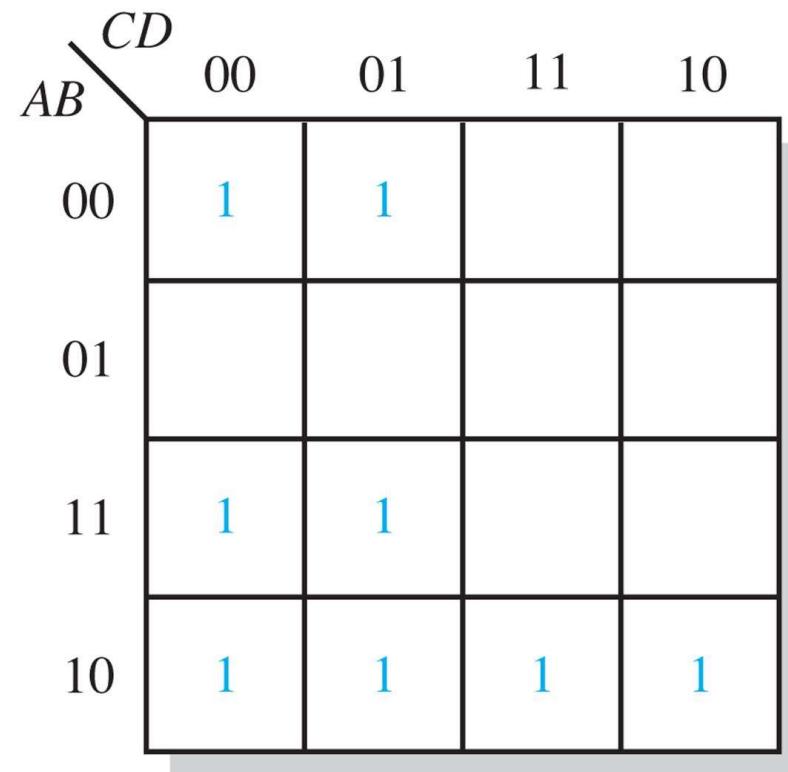
$$\overline{B}\overline{C} + A\overline{B} + AB\overline{C} + A\overline{B}C\overline{D} + \overline{A}\overline{B}\overline{C}D + A\overline{B}CD$$




Ch.4 Summary


Karnough Map Simplification

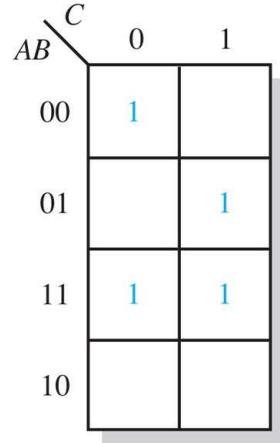


(a)

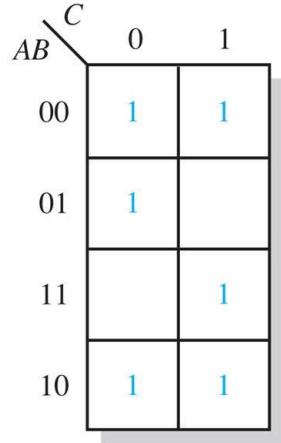

(b)

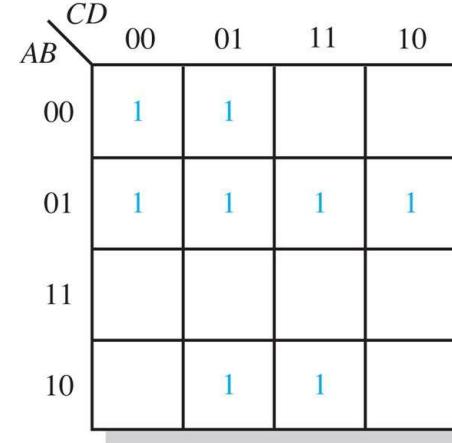

(c)

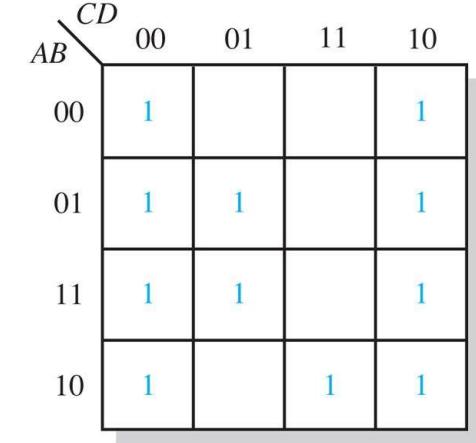


(d)


1. Group must contain 1, 2, 4, 8, 16 cells
2. Each cell in a group must be adjacent to each other
3. Always include the largest possible number of 1s

Ch.4 Summary


Karnough Map Simplification

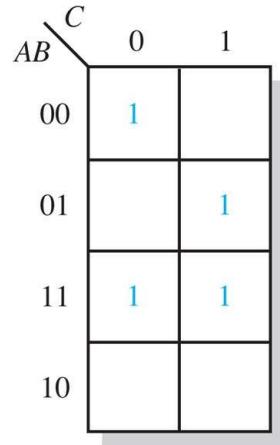


(a)

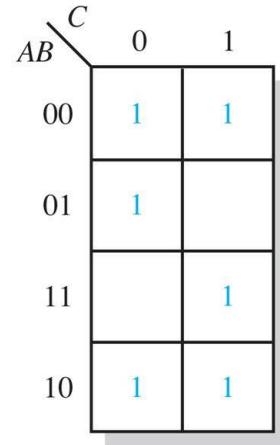


(b)

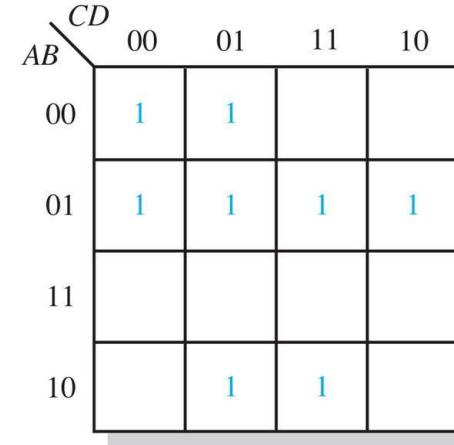


(c)

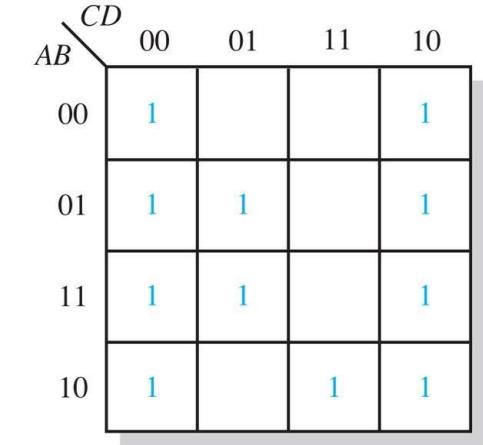


(d)

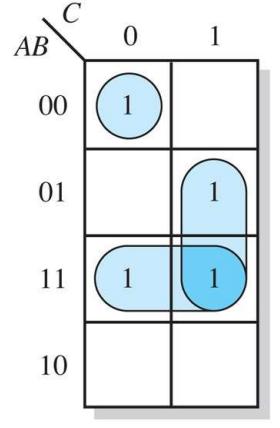


(a)

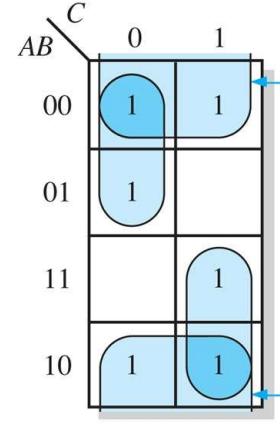

(b)

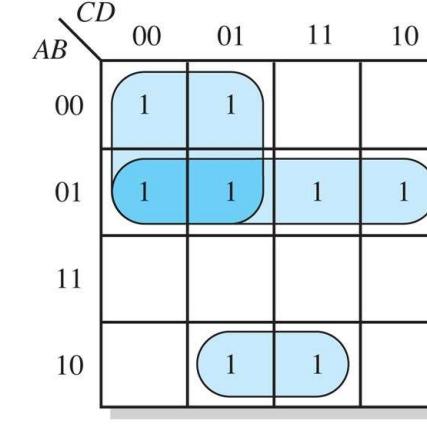


(c)

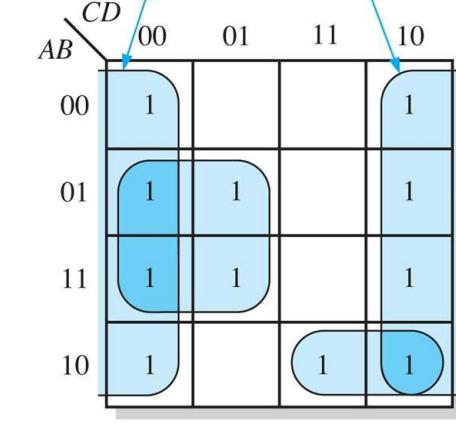


(d)

Ch.4 Summary


Karnough Map Simplification

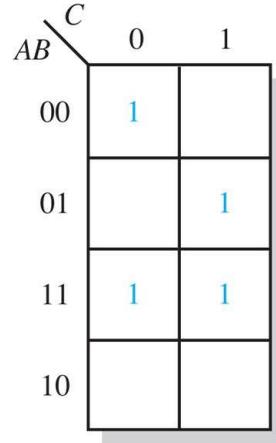


(a)

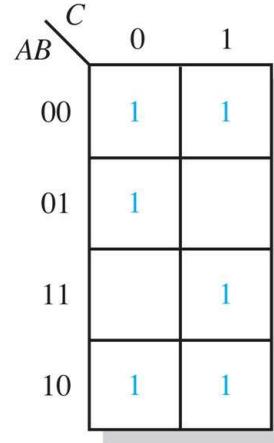





(b)

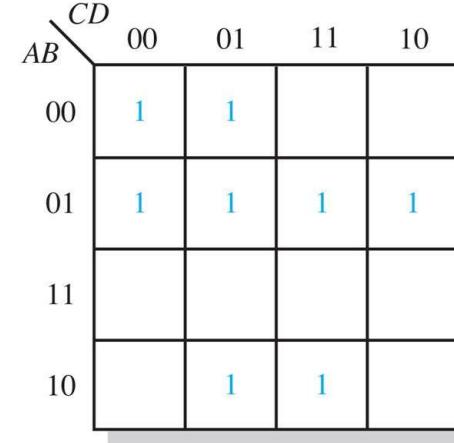

(c)

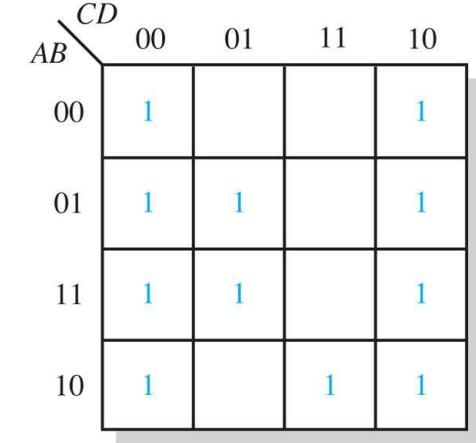

(d)

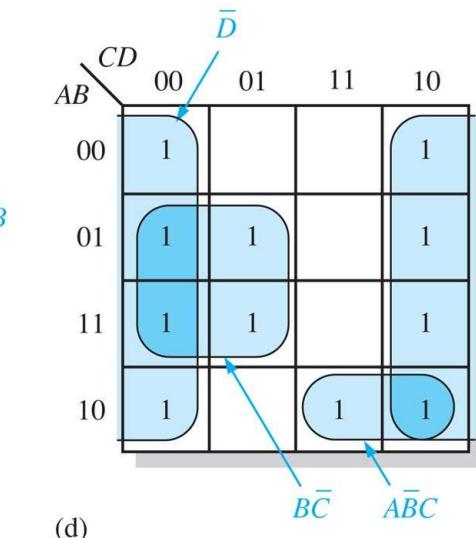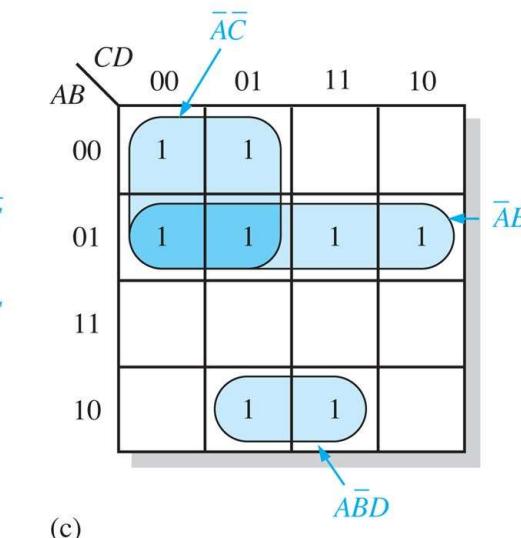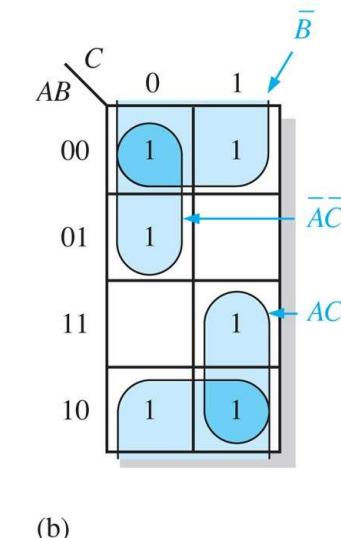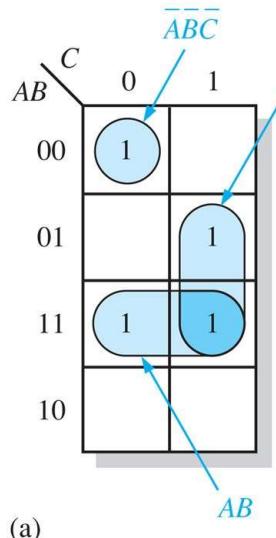


Ch.4 Summary

Karnough Map Example

$$A\bar{B}C + \bar{A}BC + \bar{A}\bar{B}C + \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C}$$

$$\downarrow$$


$$\bar{B} + \bar{A}C$$

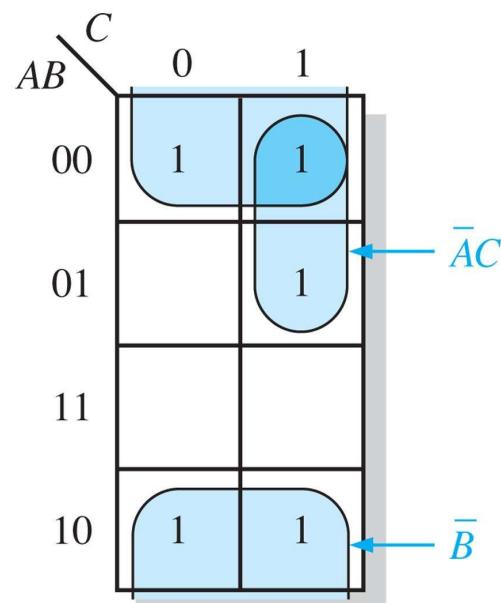

Ch.4 Summary

Karnough Map Example
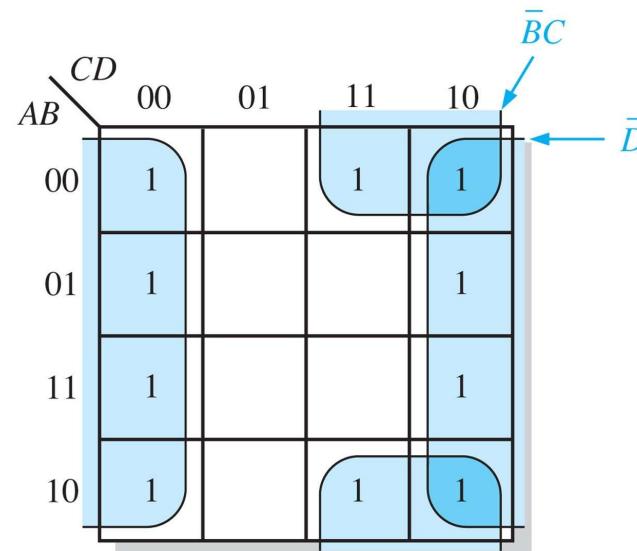
$$\begin{aligned} & \overline{BCD} + \overline{A}\overline{B}\overline{C}\overline{D} + A\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}CD + A\overline{B}CD \\ & + \overline{A}\overline{B}CD + \overline{A}\overline{B}C\overline{D} + ABC\overline{D} + A\overline{B}C\overline{D} \\ & \quad \downarrow \\ & \overline{D} + \overline{B}C \end{aligned}$$




Ch.4 Summary

Don't Care Terms

Inputs				Output
A	B	C	D	Y
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

Don't cares

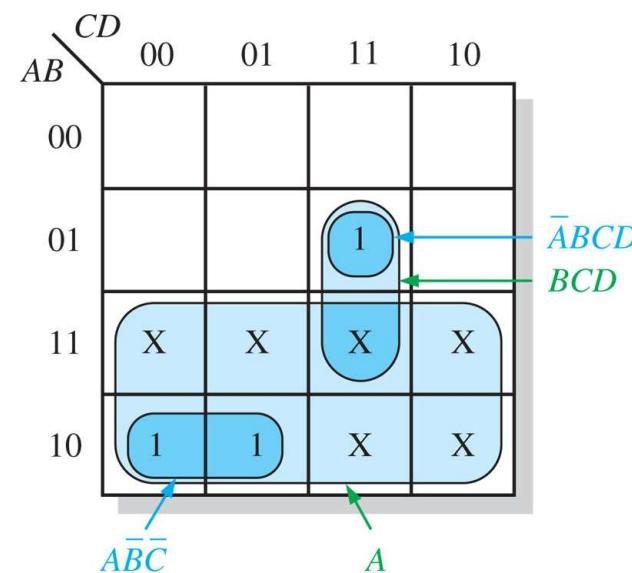


(a) Truth table

(b) Without "don't cares" $Y = \bar{A}\bar{B}\bar{C} + \bar{A}BCD$
With "don't cares" $Y = A + BCD$

Ch.4 Summary

7-Segment Display

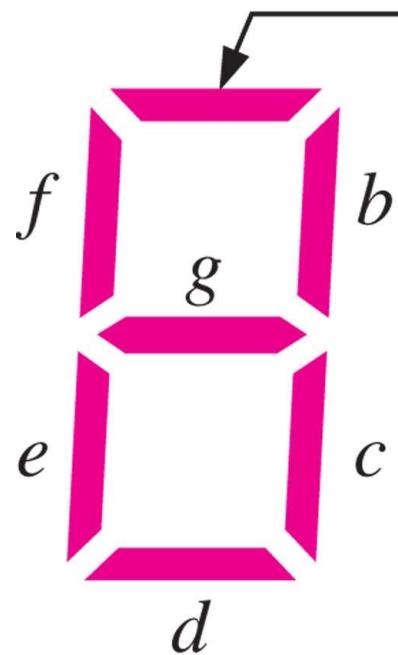

Segment *a*


0 2 3 5 6 7 8 9

$$\begin{aligned} a = & \overline{A}\overline{B}\overline{C}\overline{D} + \overline{A}\overline{B}C\overline{D} + \overline{A}\overline{B}CD + \overline{A}B\overline{C}D \\ & + \overline{A}BC\overline{D} + \overline{A}BCD + A\overline{B}\overline{C}\overline{D} + A\overline{B}\overline{C}D \end{aligned}$$

Ch.4 Summary


7-Segment Display
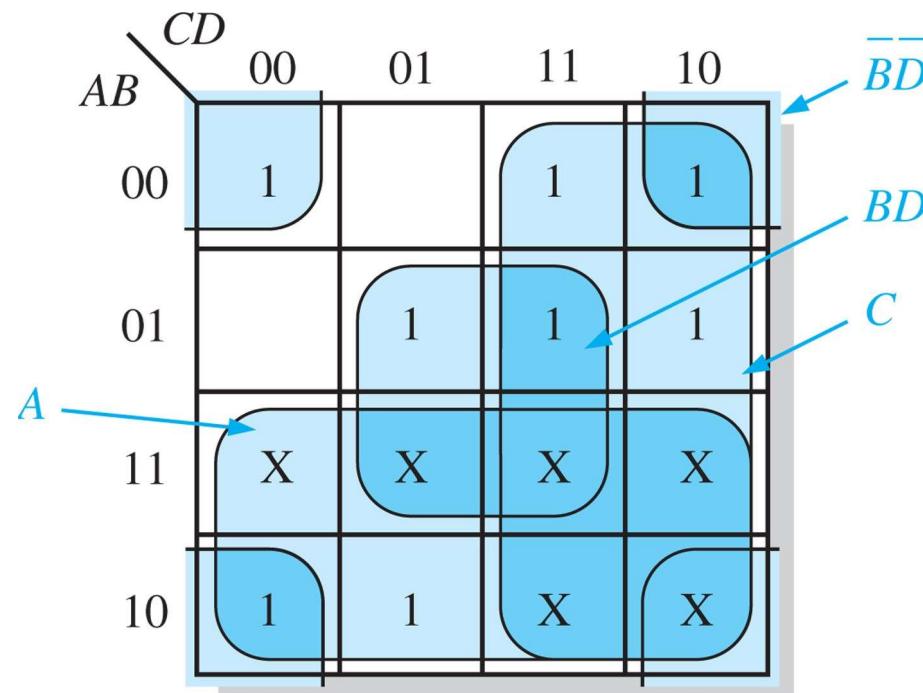
$$a = \overline{AB}\overline{CD} + \overline{AB}\overline{C}\overline{D} + \overline{AB}\overline{C}D + \overline{AB}\overline{C}\overline{D}$$
$$+ \overline{AB}\overline{C}\overline{D} + \overline{ABC}\overline{D} + A\overline{B}\overline{C}\overline{D} + A\overline{B}\overline{C}\overline{D}$$



Ch.4 Summary

Mapping a Standard POS

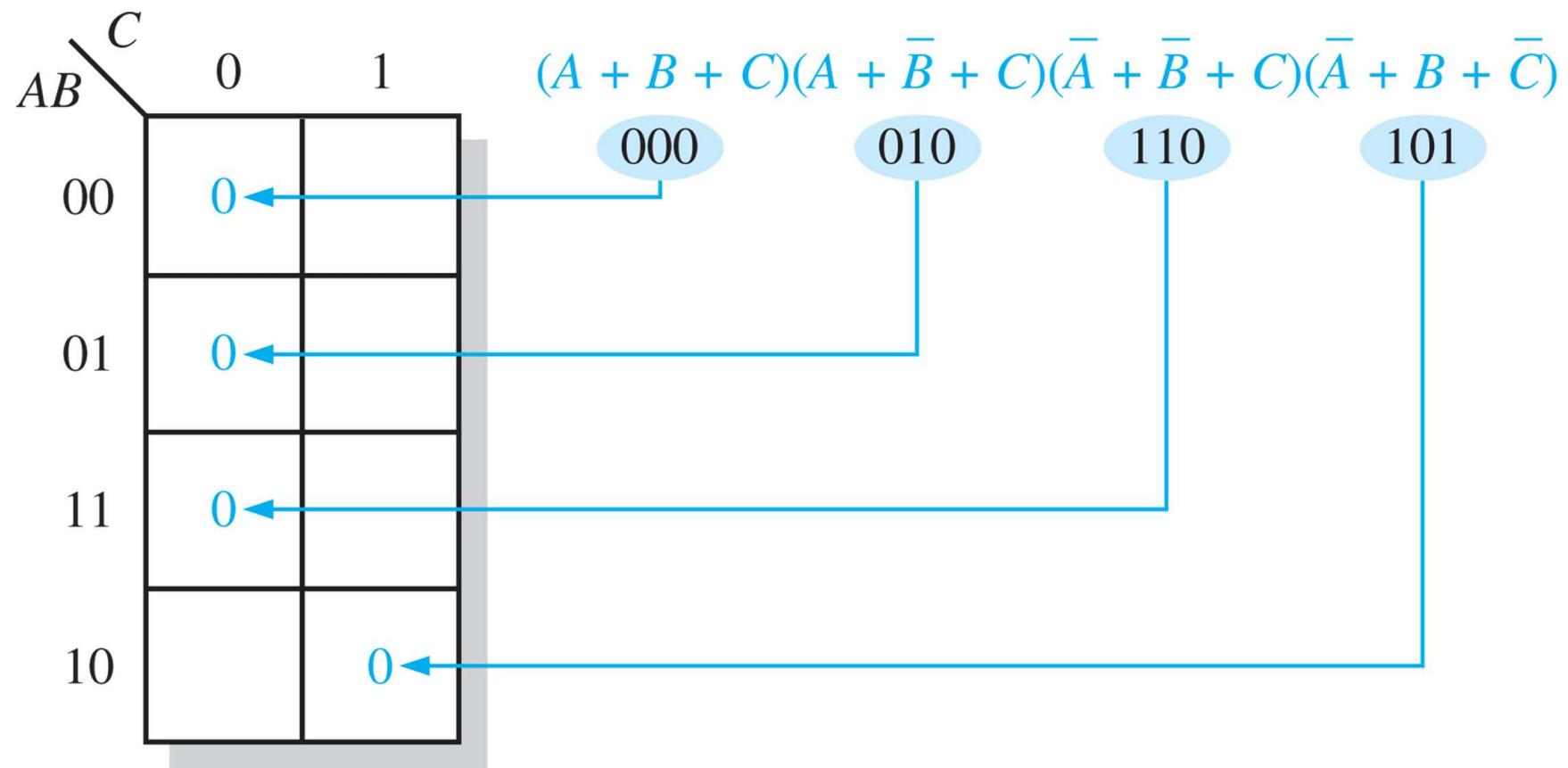


Ch.4 Summary

Mapping a Standard POS

$$(\bar{A} + \bar{B} + C + D)(\bar{A} + B + \bar{C} + \bar{D})(A + B + \bar{C} + D)$$
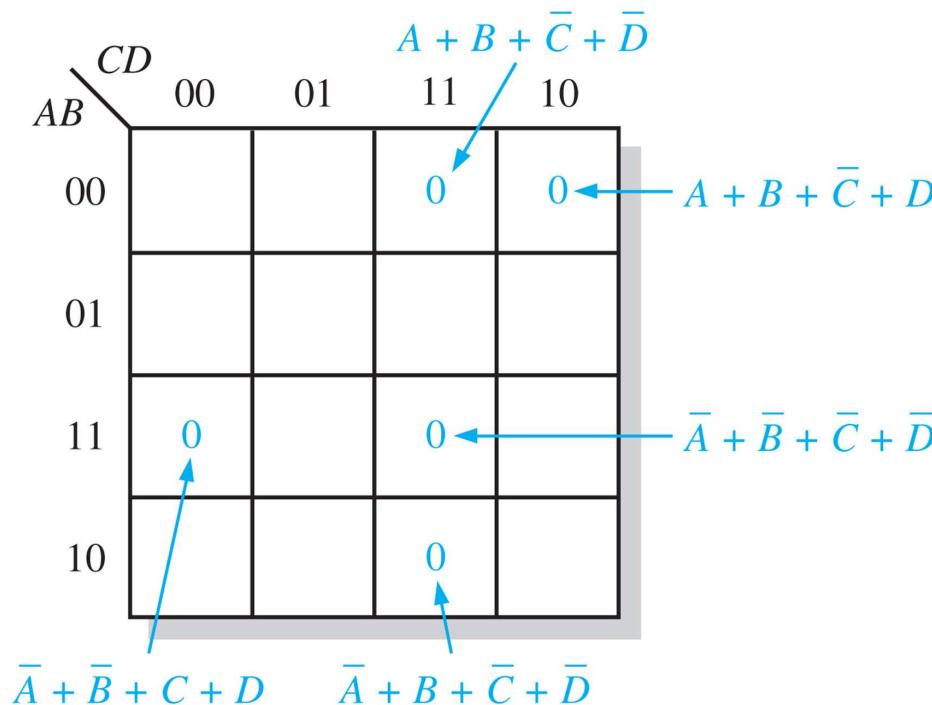
$$(\bar{A} + \bar{B} + \bar{C} + \bar{D})(A + B + \bar{C} + \bar{D})$$




Ch.4 Summary

Simplification of POS

$$(A+B+C)(A+B+\bar{C})(A+\bar{B}+C)$$
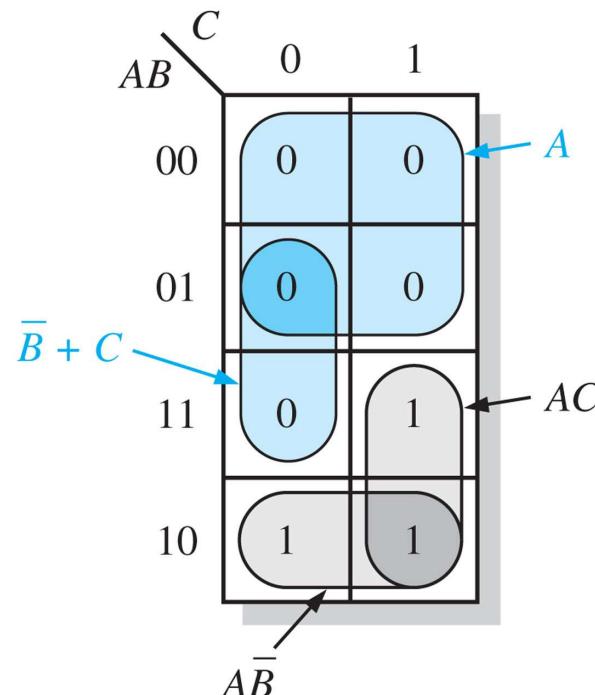
$$(A+\bar{B}+\bar{C})(\bar{A}+\bar{B}+C)$$




Ch.4 Summary

Simplification of POS

$$(B + C + D)(A + B + \bar{C} + D)(\bar{A} + B + C + \bar{D})$$
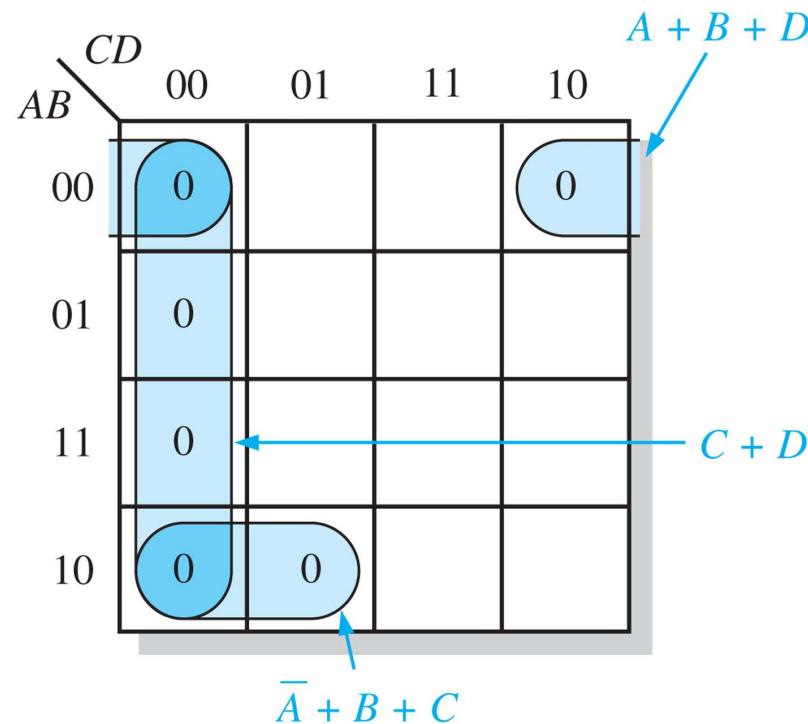
$$(A + \bar{B} + C + D)(\bar{A} + \bar{B} + C + D)$$




Ch.4 Summary

Convert between SOP and POS

$$(\bar{A} + \bar{B} + C + D)(A + \bar{B} + C + D)(A + B + C + \bar{D})$$
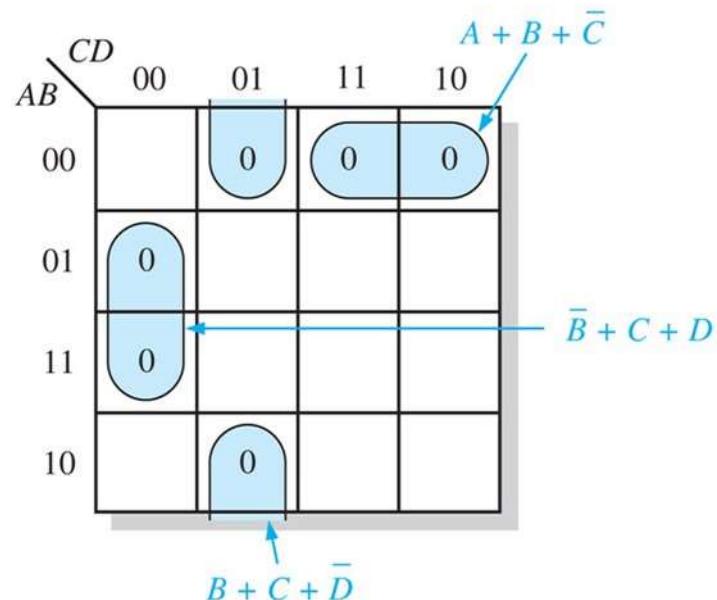
$$(A + B + \bar{C} + \bar{D})(\bar{A} + B + C + \bar{D})(A + B + \bar{C} + D)$$




(a) Minimum POS: $(A + B + \bar{C})(\bar{B} + C + D)(B + C + \bar{D})$

Ch.4 Summary


Convert between SOP and POS

$$(\bar{A} + \bar{B} + C + D)(A + \bar{B} + C + D)(A + B + C + \bar{D})$$
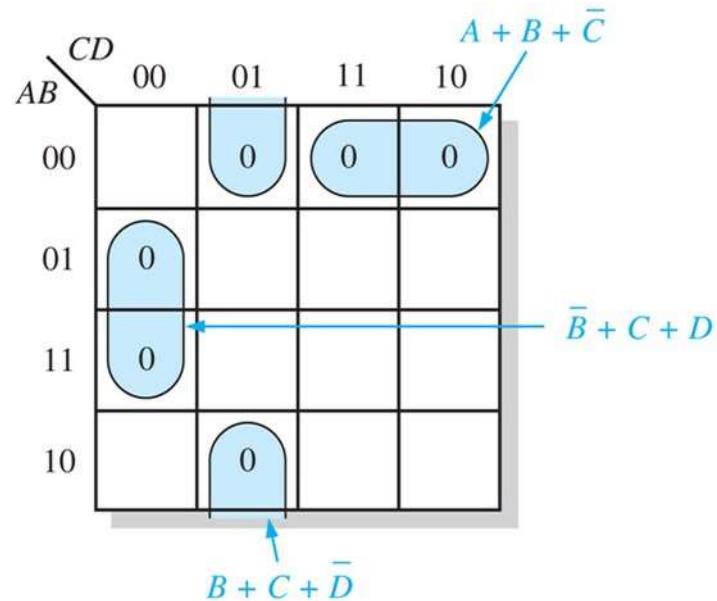
$$(A + B + \bar{C} + \bar{D})(\bar{A} + B + C + \bar{D})(A + B + \bar{C} + D)$$



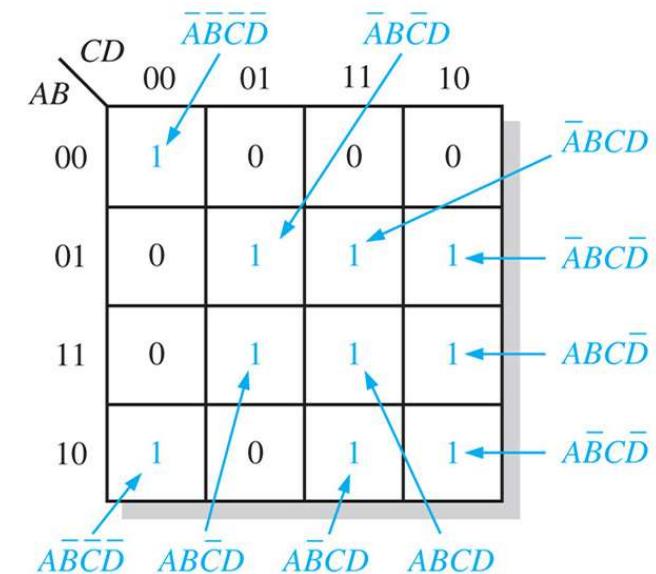(a) Minimum POS: $(A + B + \bar{C})(\bar{B} + C + D)(B + C + \bar{D})$




(b) Standard SOP:
 $\bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}B\bar{C}\bar{D} + \bar{A}B\bar{C}D + A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}D + \bar{A}\bar{B}CD + AB\bar{C}\bar{D} + ABC\bar{D}$

Ch.4 Summary


Convert between SOP and POS

$$(\bar{A} + \bar{B} + C + D)(A + \bar{B} + C + D)(A + B + C + \bar{D})$$
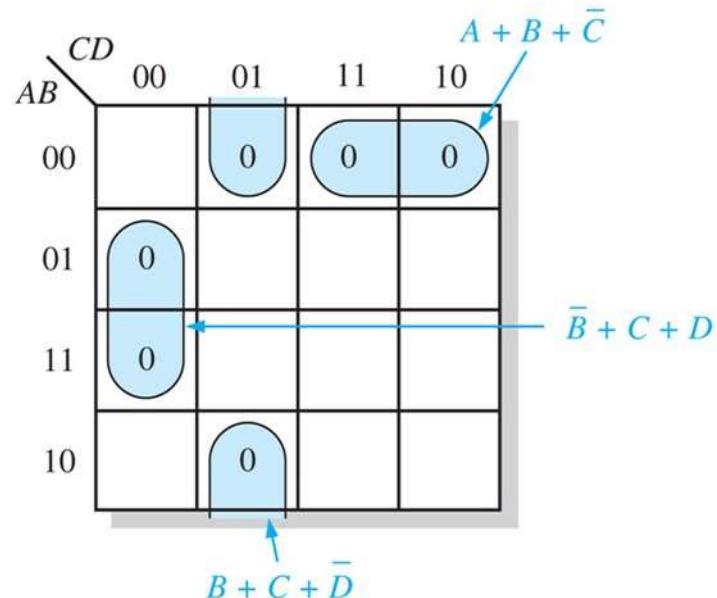
$$(A + B + \bar{C} + \bar{D})(\bar{A} + B + C + \bar{D})(A + B + \bar{C} + D)$$



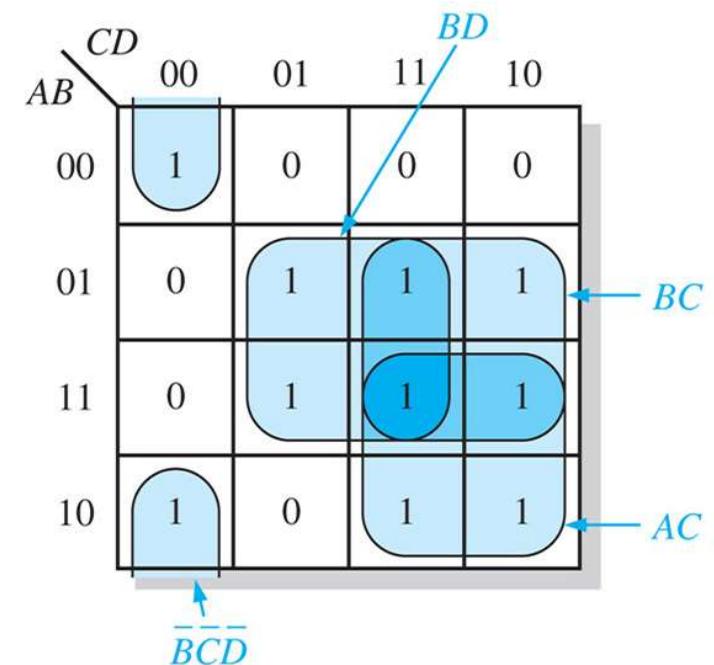(a) Minimum POS: $(A + B + \bar{C})(\bar{B} + C + D)(B + C + \bar{D})$



(c) Minimum SOP: $AC + BC + BD + \bar{BC}\bar{D}$

Ch.4 Summary

Quine-McCluskey Method

TABLE 4-9

<i>ABCD</i>	<i>X</i>	Minterm
0000	0	
0001	1	m_1
0010	0	
0011	1	m_3
0100	1	m_4
0101	1	m_5
0110	0	
0111	0	
1000	0	
1001	0	
1010	1	m_{10}
1011	0	
1100	1	m_{12}
1101	1	m_{13}
1110	0	
1111	1	m_{15}

Ch.4 Summary

Quine-McCluskey Method

TABLE 4-10

Number of 1s	Minterm	<i>ABCD</i>
1	m_1	0001
	m_4	0100
2	m_3	0011
	m_5	0101
	m_{10}	1010
	m_{12}	1100
	m_{13}	1101
3		
4	m_{15}	1111

Ch.4 Summary

Quine-McCluskey Method

TABLE 4-11

Number of 1s in Minterm	Minterm	ABCD	First Level
1	m_1	0001 ✓	(m_1, m_3) 00x1
	m_4	0100 ✓	(m_1, m_5) 0x01
2	m_3	0011 ✓	(m_4, m_5) 010x
	m_5	0101 ✓	(m_4, m_{12}) x100
	m_{10}	1010	(m_5, m_{13}) x101
	m_{12}	1100 ✓	(m_{12}, m_{13}) 110x
3	m_{13}	1101 ✓	(m_{13}, m_{15}) 11x1
4	m_{15}	1111 ✓	

Ch.4 Summary

Quine-McCluskey Method

TABLE 4-12

First Level	Number of 1s in First Level	Second Level
$(m_1, m_3) \ 00x1$	1	$(m_4, m_5, m_{12}, m_{13}) \ x10x$
$(m_1, m_5) \ 0x01$		$(m_4, m_5, m_{12}, m_{13}) \ x10x$
$(m_4, m_5) \ 010x \checkmark$		
$(m_4, m_{12}) \ x100 \checkmark$		
$(m_5, m_{13}) \ x101 \checkmark$	2	
$(m_{12}, m_{13}) \ 110x \checkmark$		
$(m_{13}, m_{15}) \ 11x1$	3	

Ch.4 Summary


Quine-McCluskey Method

TABLE 4-13


Prime Implicants	Minterms							
	m_1	m_3	m_4	m_5	m_{10}	m_{12}	m_{13}	m_{15}
$B\bar{C} (m_4, m_5, m_{12}, m_{13})$			✓	✓		✓	✓	
$\bar{A}\bar{B}D (m_1, m_3)$	✓	✓						
$\bar{A}\bar{C}D (m_1, m_5)$	✓			✓				
$ABD (m_{13}, m_{15})$							✓	✓
$A\bar{B}\bar{C}\bar{D} (m_{10})$						✓		

Ch.4 Summary

7-Segment Display

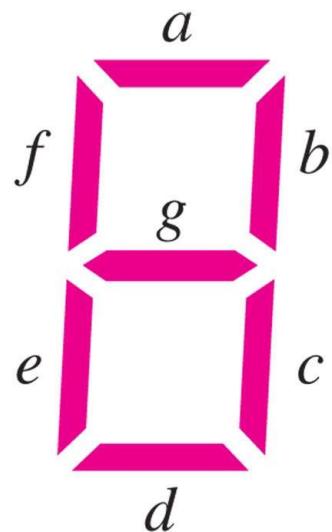


(a) Segment arrangement

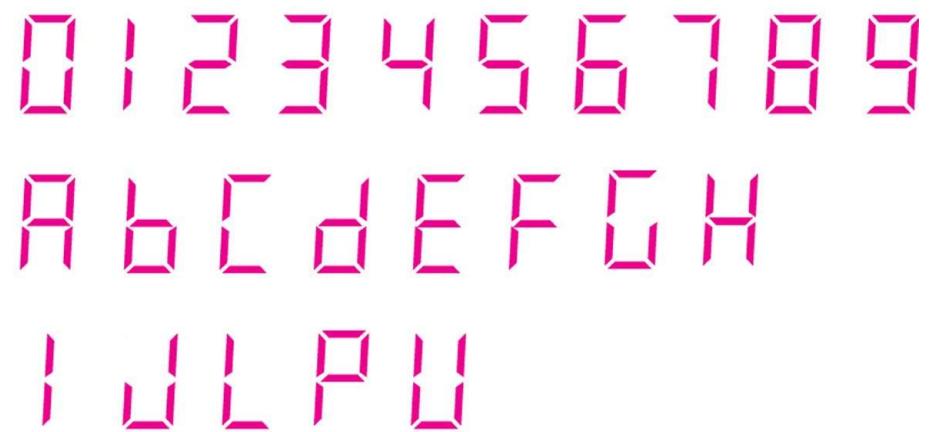

(b) Formation of the ten digits
and certain letters

Ch.4 Summary

7-Segment Display

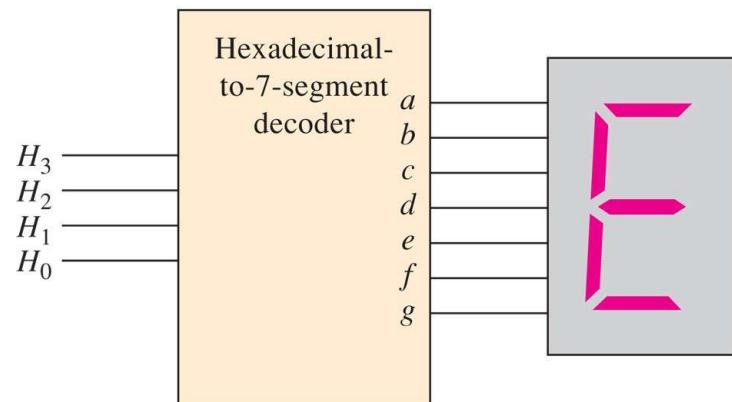

(a)


Letter	Hexadecimal Inputs				Segment Outputs						
	H_3	H_2	H_1	H_0	a	b	c	d	e	f	g
A	1	0	1	0	0	0	0	1	0	0	0
b	1	0	1	1	1	1	0	0	0	0	0
C	1	1	0	0	0	1	1	0	0	0	1
d	1	1	0	1	1	0	0	0	0	1	0
E	1	1	1	0	0	1	1	0	0	0	0
F	1	1	1	1	1	1	1	1	1	1	1

(b)


1. Display the type of Vitamin (A, b, C, d, E)
2. F is not used as an Input

Ch.4 Summary


7-Segment Display

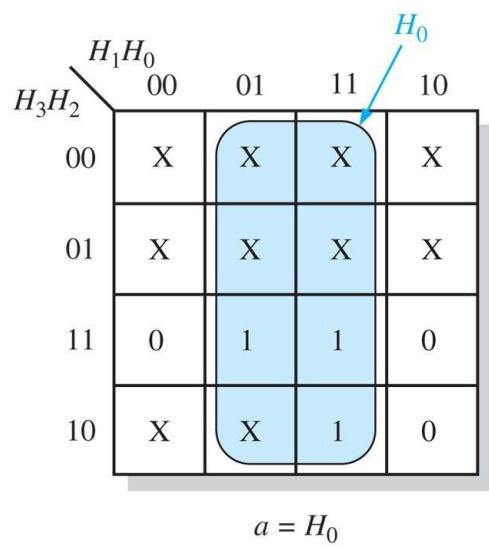

(a)

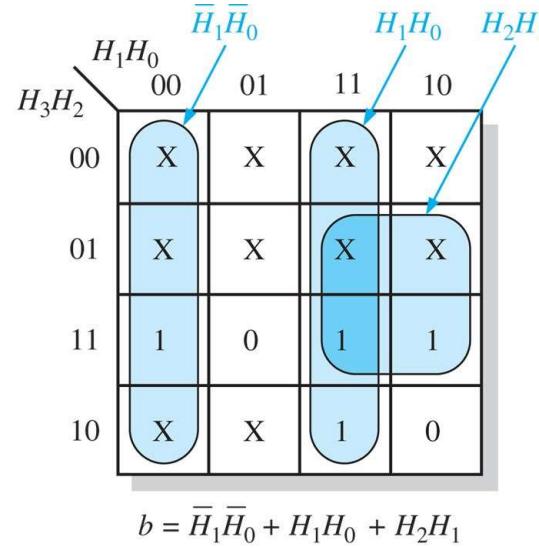

(b)

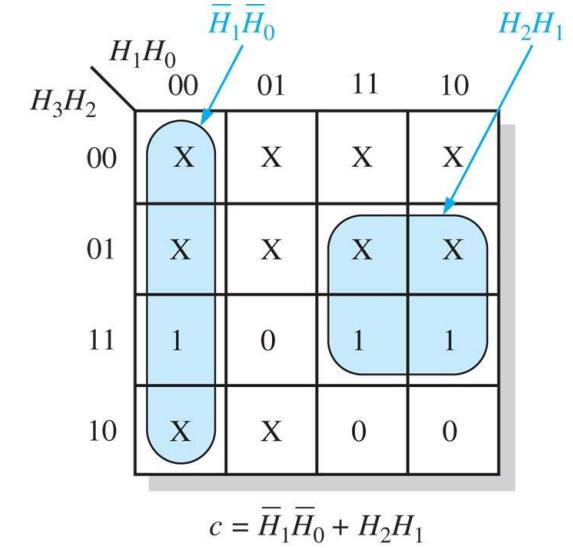

(c)