

Digital Fundamentals


Thomas L. Floyd

Latches, Flip-Flops, and Timers
Chapter 7

Ch.7 Summary

Latches

 A **latch** is a temporary storage device that has two stable states (bistable). It is a basic form of memory.



The S-R (Set-Reset) latch is the most basic type. It can be constructed from NOR gates or NAND gates. With NOR gates, the latch responds to active-HIGH inputs; with NAND gates, it responds to active-LOW inputs.


Ch.7 Summary

Latches

The active-HIGH S-R latch is in a stable (latched) condition when both inputs are LOW.

Assume the latch is initially RESET ($Q = 0$) and the inputs are at their inactive level (0). To SET the latch ($Q = 1$), a momentary HIGH signal is applied to the S input while the R remains LOW.

 To RESET the latch ($Q = 0$), a momentary HIGH signal is applied to the R input while the S remains LOW.




Ch.7 Summary

Latches

The active-LOW \bar{S} - \bar{R} latch is in a stable (latched) condition when both inputs are HIGH.

Assume the latch is initially RESET ($Q = 0$) and the inputs are at their inactive level (1). To SET the latch ($Q = 1$), a momentary LOW signal is applied to the \bar{S} input while the \bar{R} remains HIGH.

 To RESET the latch a momentary LOW is applied to the \bar{R} input while \bar{S} is HIGH.



Never apply an active set and reset at the same time (invalid).

Ch.7 Summary

Latches

 


TABLE 7-1


Truth table for an active-LOW input \bar{S} - \bar{R} latch.

Inputs		Outputs		Comments
\bar{S}	\bar{R}	Q	\bar{Q}	
1	1	NC	NC	No change. Latch remains in present state.
0	1	1	0	Latch SET.
1	0	0	1	Latch RESET.
0	0	1	1	Invalid condition

Ch.7 Summary


Latches

The three modes of basic S-R operation

 


Ch.7 Summary

Latches

 



(a) Active-HIGH input
S-R latch

 

(b) Active-LOW input
 \bar{S} - \bar{R} latch


Ch.7 Summary

Latches

  


Ch.7 Summary

Latches: Applications

 

(a) Switch contact bounce

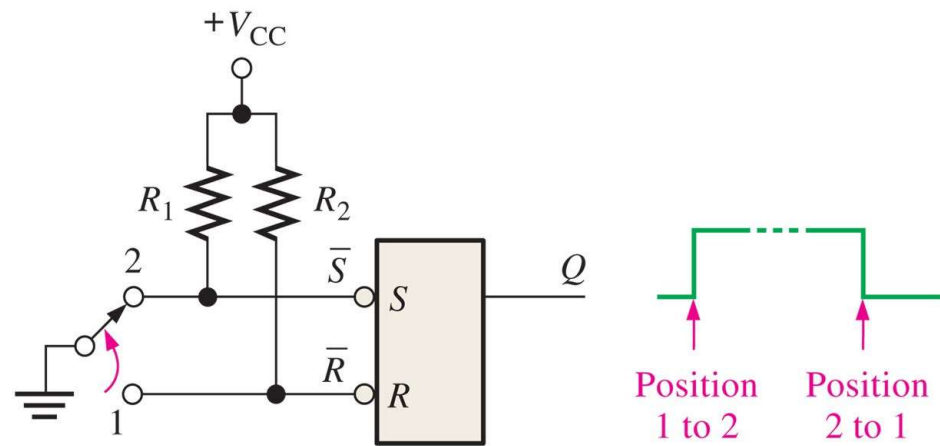


(b) Contact-bounce eliminator circuit

Ch.7 Summary

Gated S-R Latch


A gated latch is a variation on the basic latch.

 The gated latch has an additional input, called enable (EN) that must be HIGH in order for the latch to respond to the S and R inputs.



Ch.7 Summary


Gated S-R Latch

 

Ch.7 Summary

Gated D Latch

 The D latch is an variation of the S - R latch but combines the S and R inputs into a single D input as shown:



A simple rule for the D latch is:


Q follows D when the EN is active.

Ch.7 Summary

Flip-flops

A flip-flop differs from a latch in the manner it changes states. A flip-flop is a clocked device, in which only the clock edge determines when a new bit is entered.

 The active edge can be positive or negative.




Ch.7 Summary

Edge-Triggered Flip-flops

The output from an edge-triggered flip-flop changes on the positive-going or negative-going edge of its clock signal.

 
A bubble on the clock input indicates that it is a negative-edge triggered flip-flop.



Ch.7 Summary

Edge-Triggered D Flip-flops

 
The data bit at the D-input is transferred to the component output on the edge of the clock signal.



Once triggered, the output (Q) equals the last value at the D input until a new value is triggered in.

Ch.7 Summary


Edge-Triggered D Flip-flops

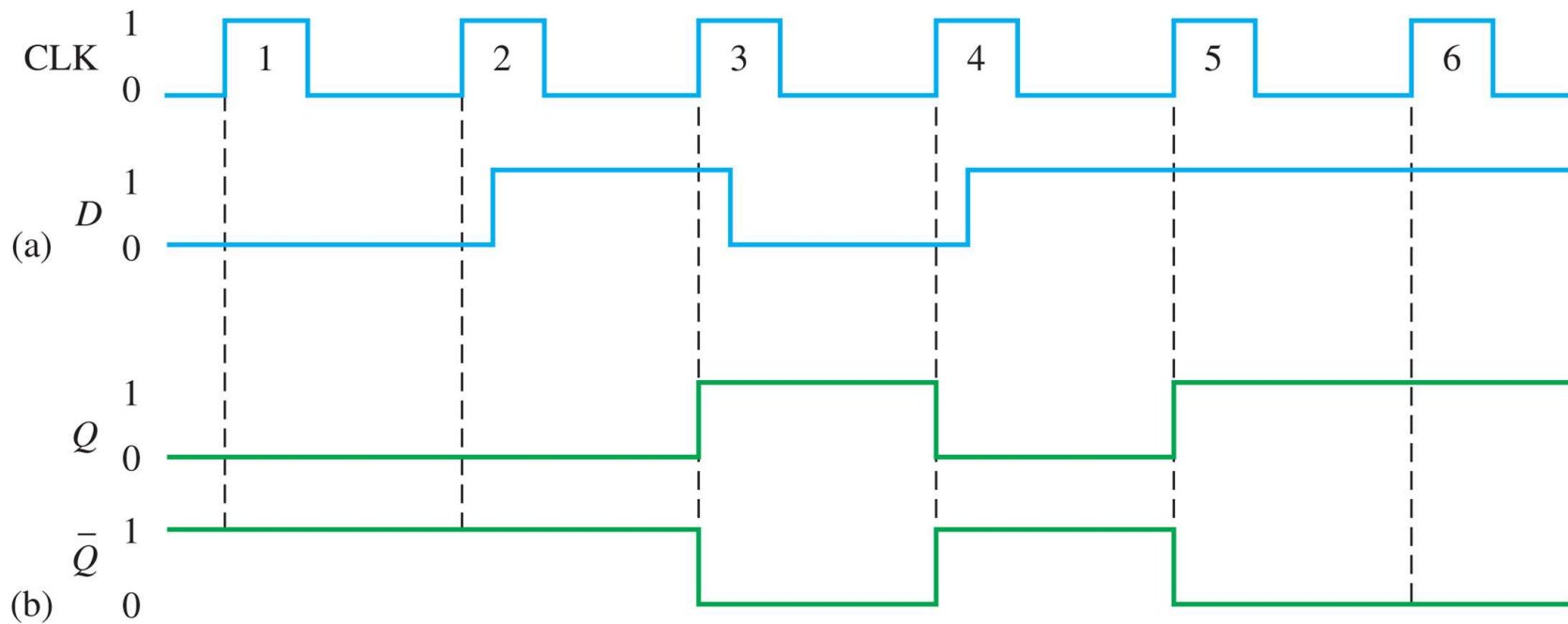

Ch.7 Summary

J-K Flip-flops

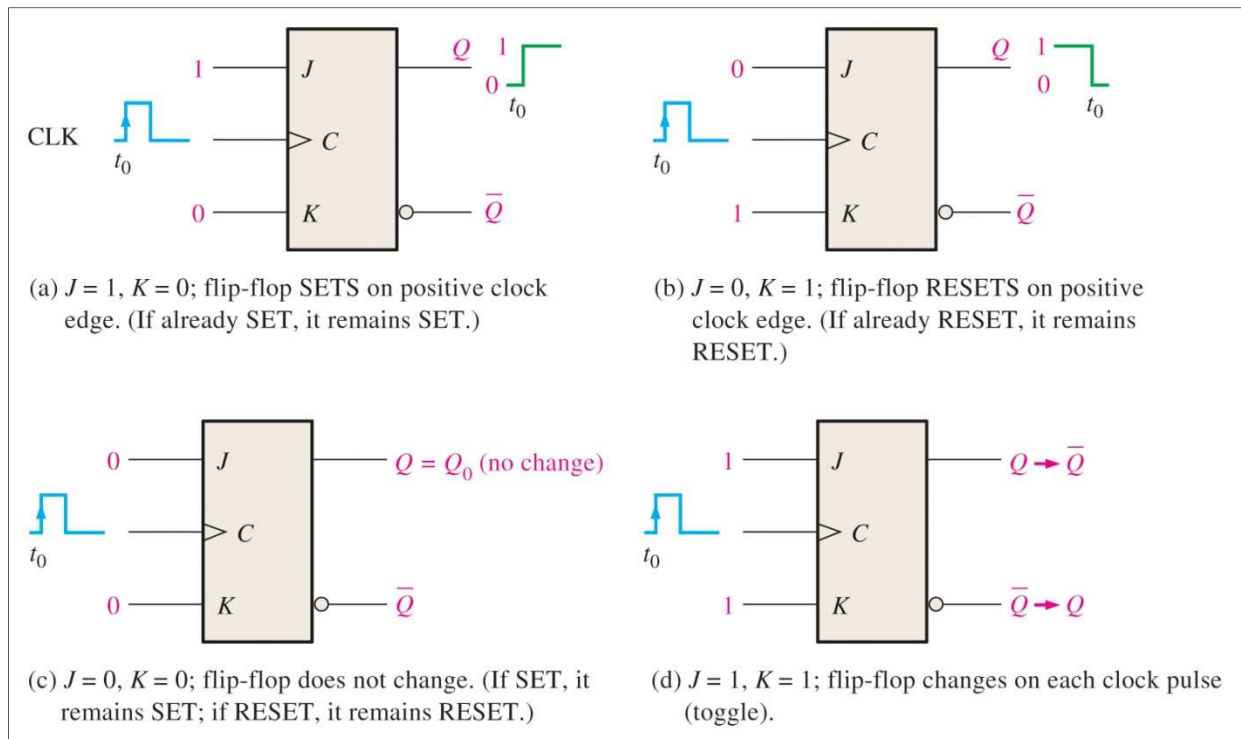The values at the J and K inputs to a J-K flip-flop determine its output state. The results of the four possible input combinations of J and K are shown.



Ch.7 Summary

J-K Flip-flops

TABLE 7-3

Truth table for a positive edge-triggered J-K flip-flop.



Inputs			Outputs		Comments
<i>J</i>	<i>K</i>	CLK	<i>Q</i>	\overline{Q}	
0	0	↑	Q_0	\overline{Q}_0	No change
0	1	↑	0	1	RESET
1	0	↑	1	0	SET
1	1	↑	\overline{Q}_0	Q_0	Toggle

↑ = clock transition LOW to HIGH

Q_0 = output level prior to clock transition


Ch.7 Summary

J-K Flip-flops

 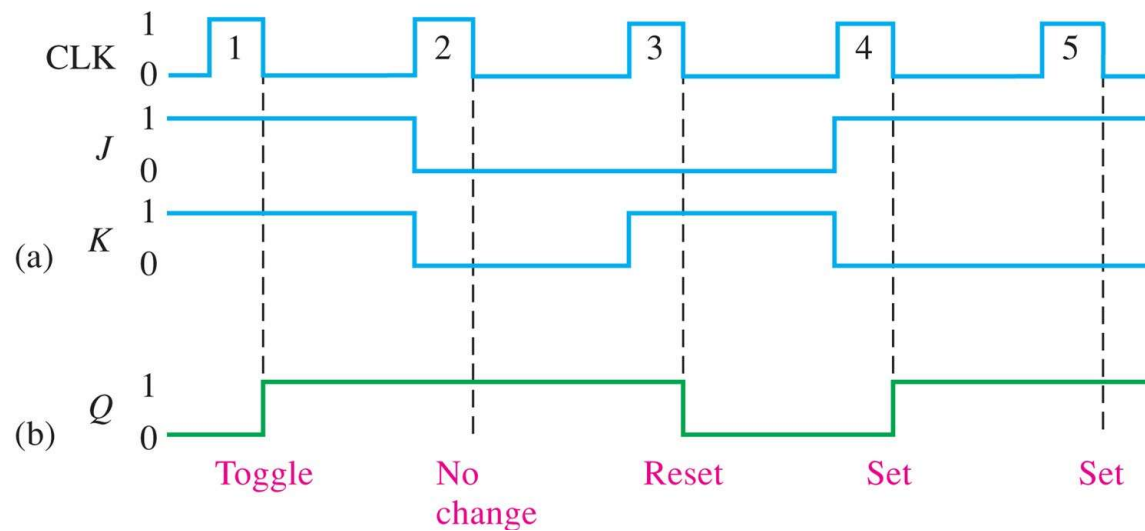


Ch.7 Summary

Edge Triggered Operation

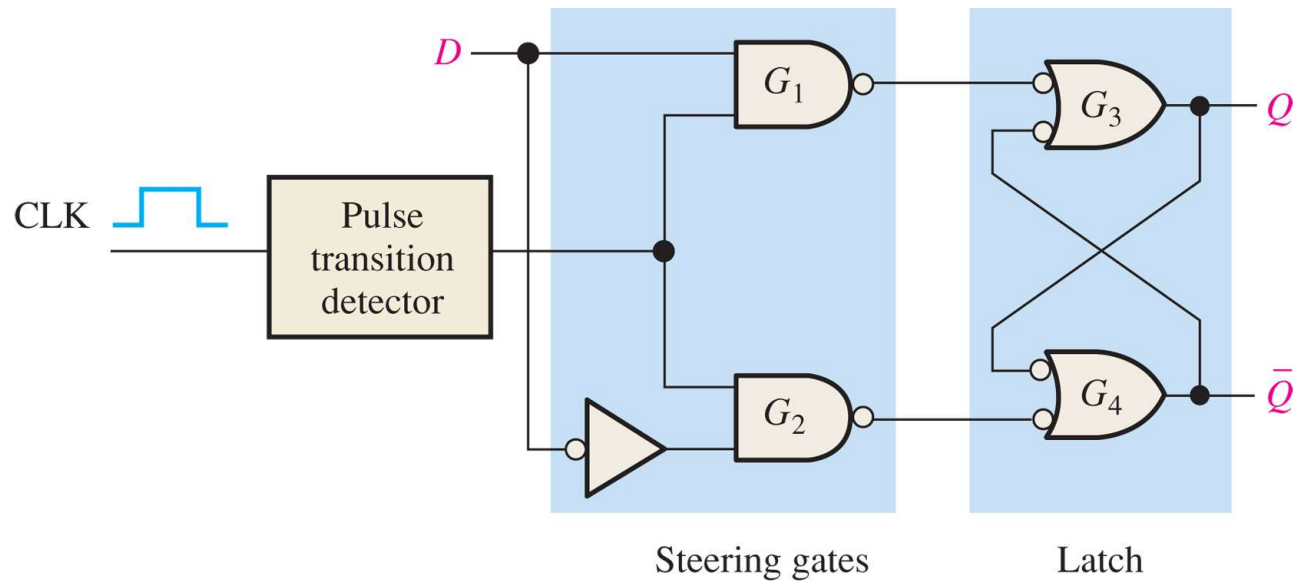

 
(a) A simplified logic diagram for a positive edge-triggered D flip-flop



(b) A type of pulse transition detector


Ch.7 Summary

D Flip-flops

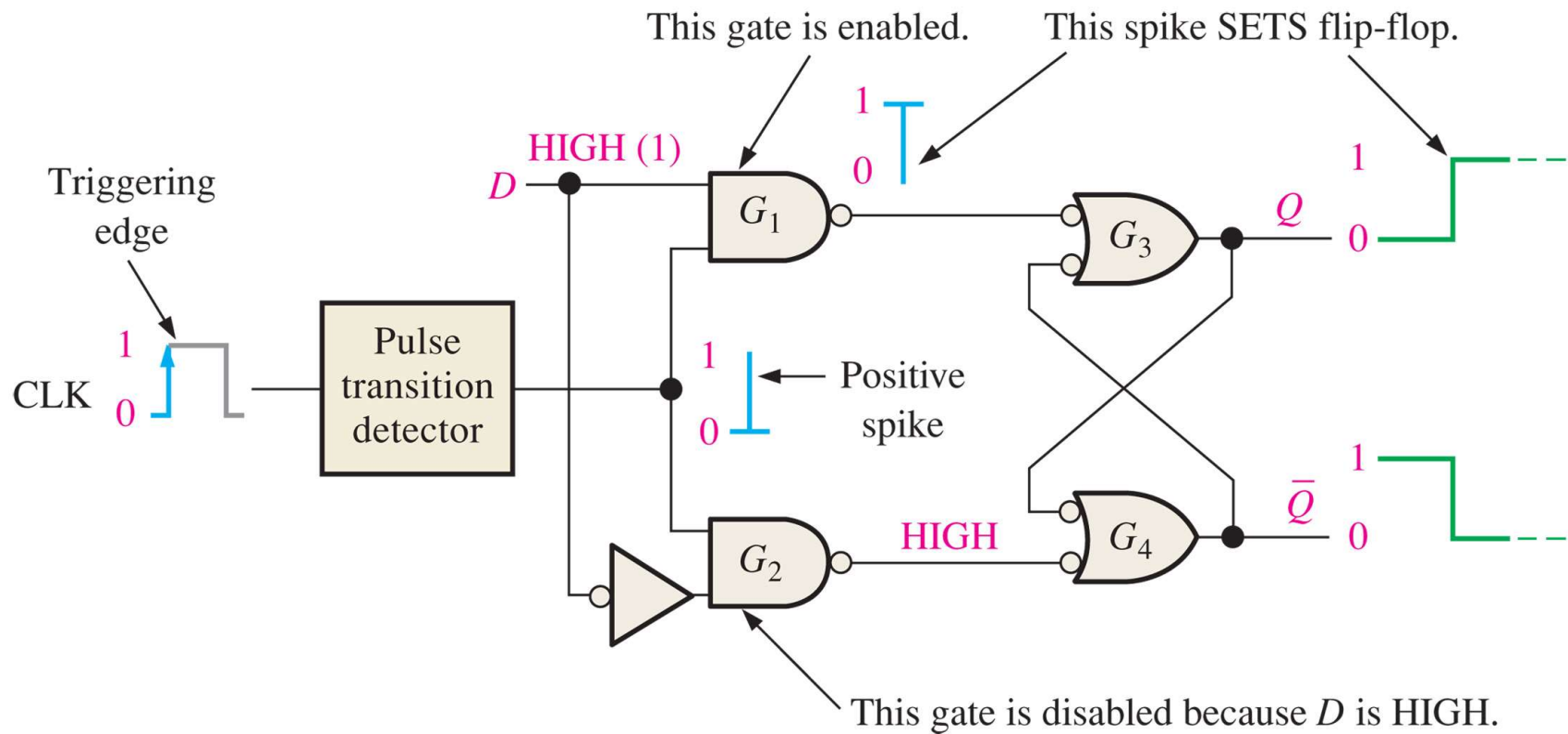


Ch.7 Summary

D Flip-flops

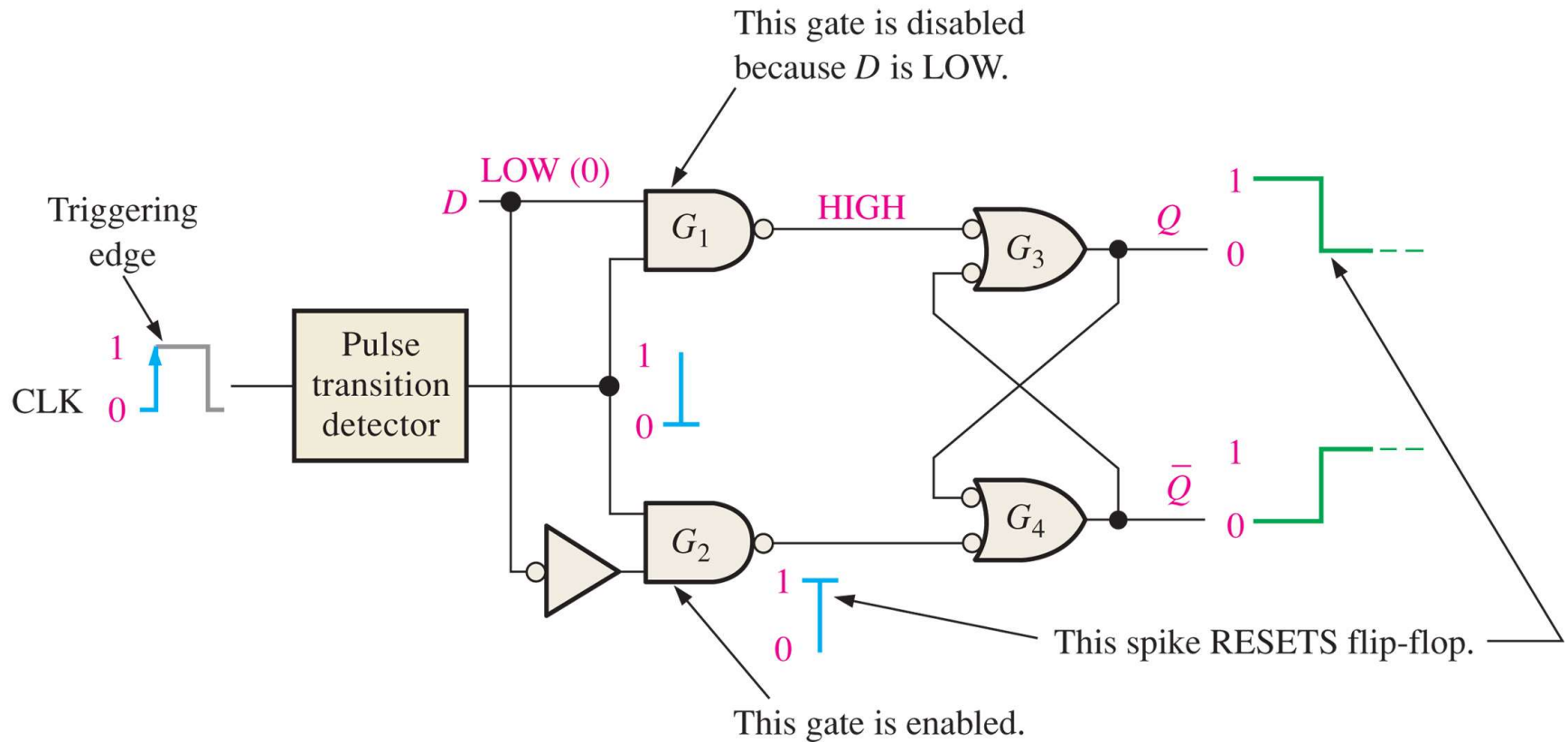


Ch.7 Summary

J-K Flip-flops

 

Ch.7 Summary

J-K Flip-flops

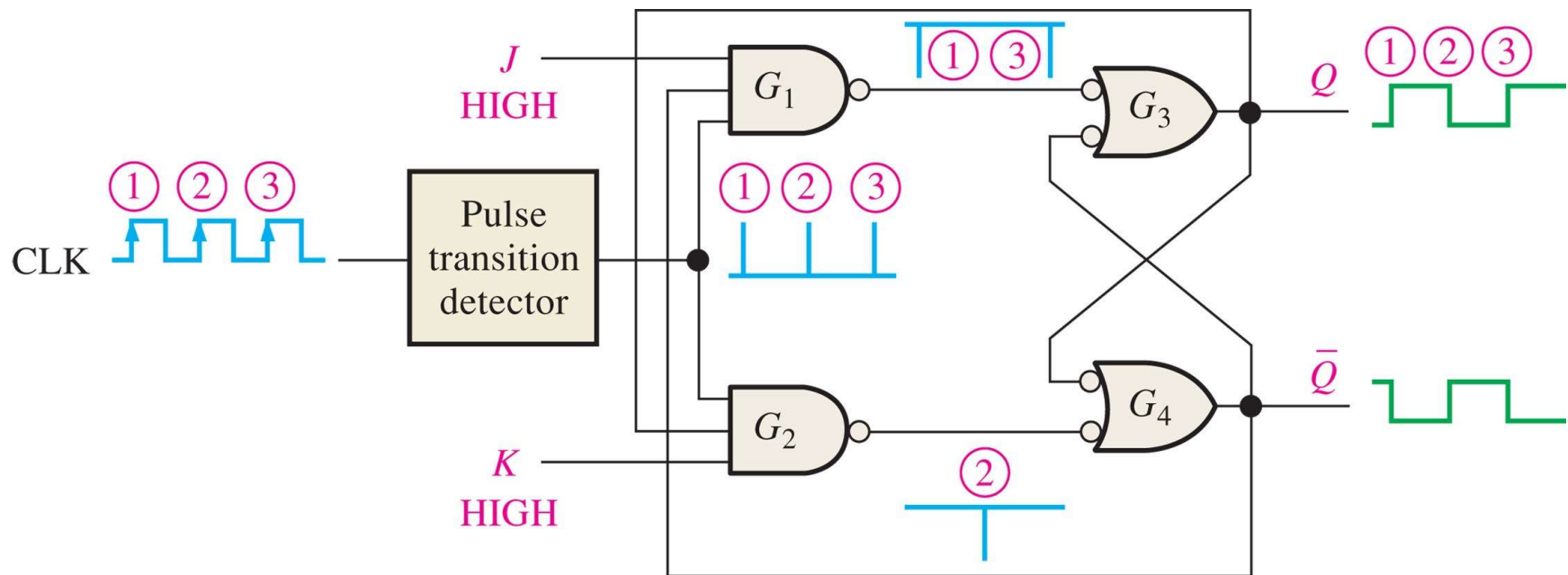


Ch.7 Summary

Flip-flop Asynchronous Inputs

Synchronous (clocked) inputs are transferred on the triggering edge of the clock. Most flip-flops have other inputs that are **asynchronous**, meaning they operate independently of the clock.



Asynchronous flip-flop inputs are normally labeled preset (\overline{PRE}) and clear (\overline{CLR}). These inputs are usually active LOW. A J-K flip flop with active LOW preset and CLR is shown.

 Note that the asynchronous inputs always override the synchronous inputs.



Ch.7 Summary


Flip-flop Asynchronous Inputs

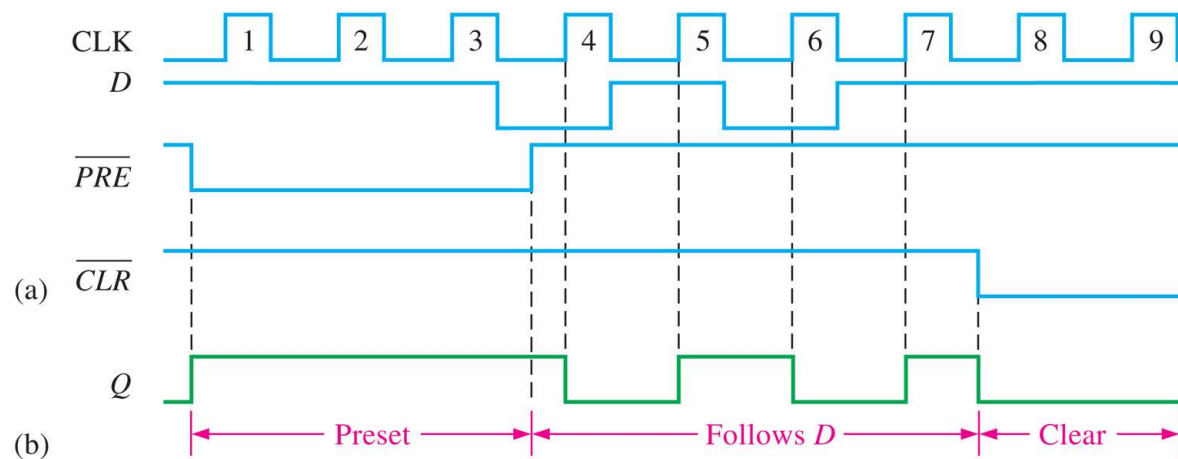 

Ch.7 Summary

Flip-Flop Propagation Delay

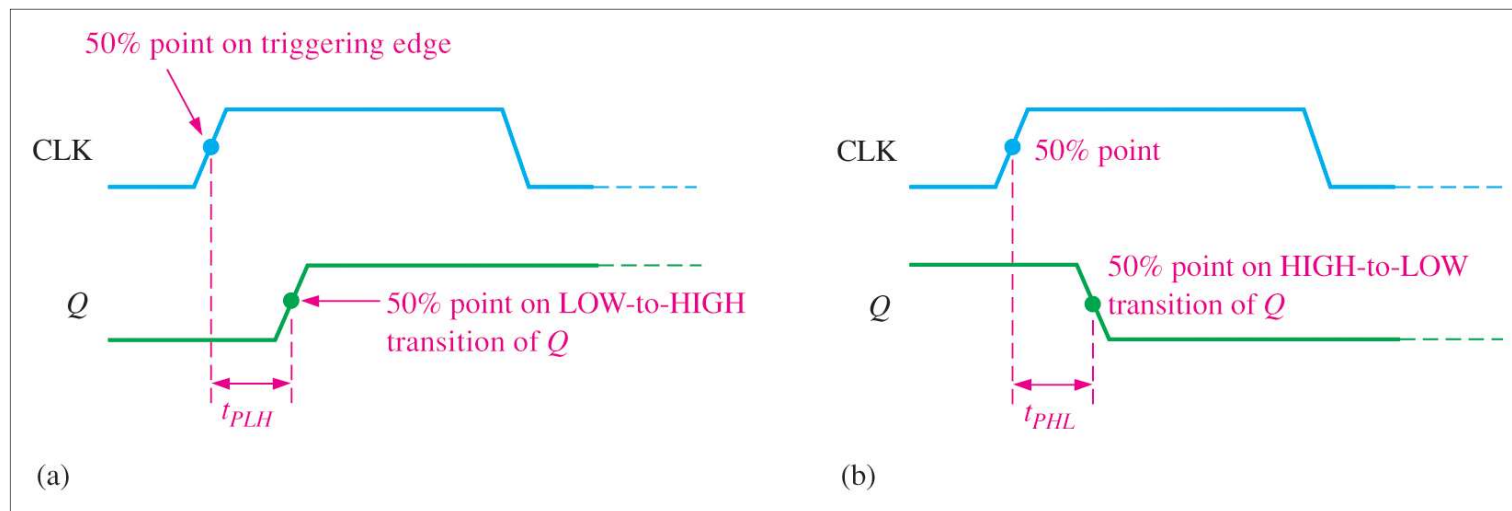Propagation delay time is specified for the rising and falling outputs. It is measured between the 50% level of the clock to the 50% level of the output transition.




Propagation delay (t_{PLH}) is measured as shown in (a). Propagation delay (t_{PHL}) is measured as shown in (b).

Ch.7 Summary

Flip-flop Propagation Delay

 
Another **propagation delay time** specification is the time required for an *asynchronous input* to cause a change in the output. Again it is measured from the 50% levels.



Ch.7 Summary

Flip-flop Set-up Time

 
Another time-related specification is flip-flop **set-up time**. This is the minimum time between the arrival of an input to the D (or J-K) flip-flop and the CLK signal.



Ch.7 Summary

Flip-flop Hold Time

 
Another time-related specification is flip-flop **hold time**. This is the minimum time over which the input to the D (or J-K) flip-flop must remain stable *after* the arrival of the CLK input for reliable triggering.



Ch.7 Summary

Flip-Flop Frequency Division

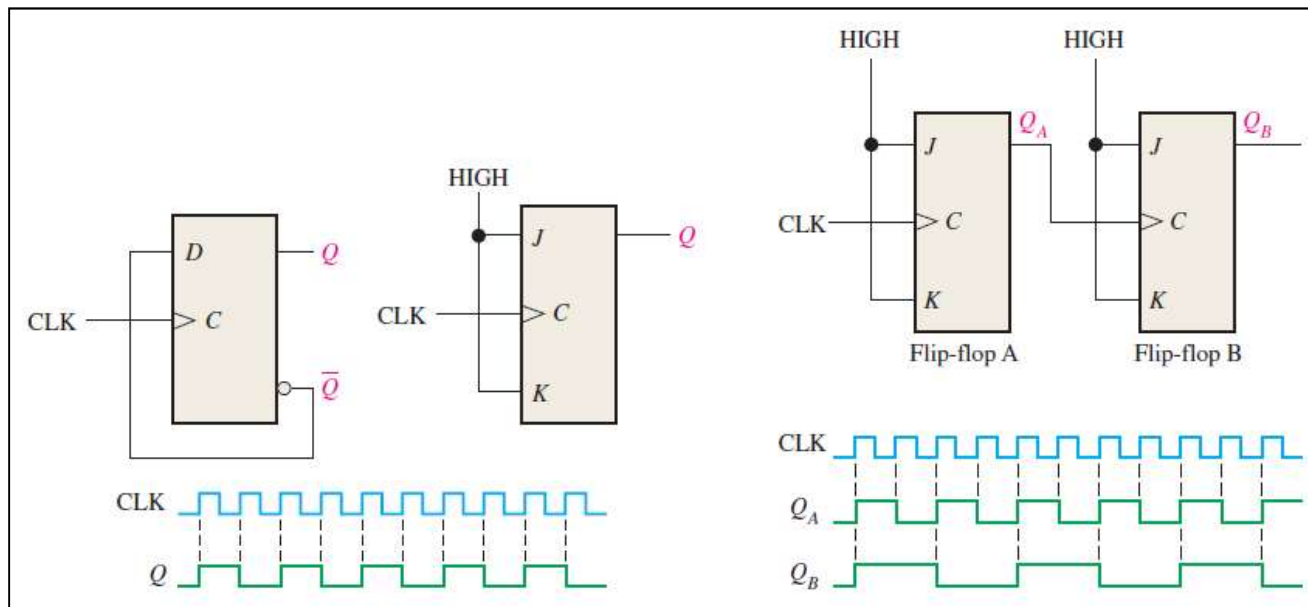Flip-flops can be used as frequency dividers, as shown below.



The D and J-K flip flops on the left are wired as “divide-by-2” circuits.

The J-K flip-flops on the right are cascaded to form a “divide-by-4” circuit.


Ch.7 Summary

Flip-Flop Counters

Flip-flops can be used to count the number of clock signals they receive as shown here.

Each CLK input triggers the flip-flops, which are wired to toggle whenever triggered.

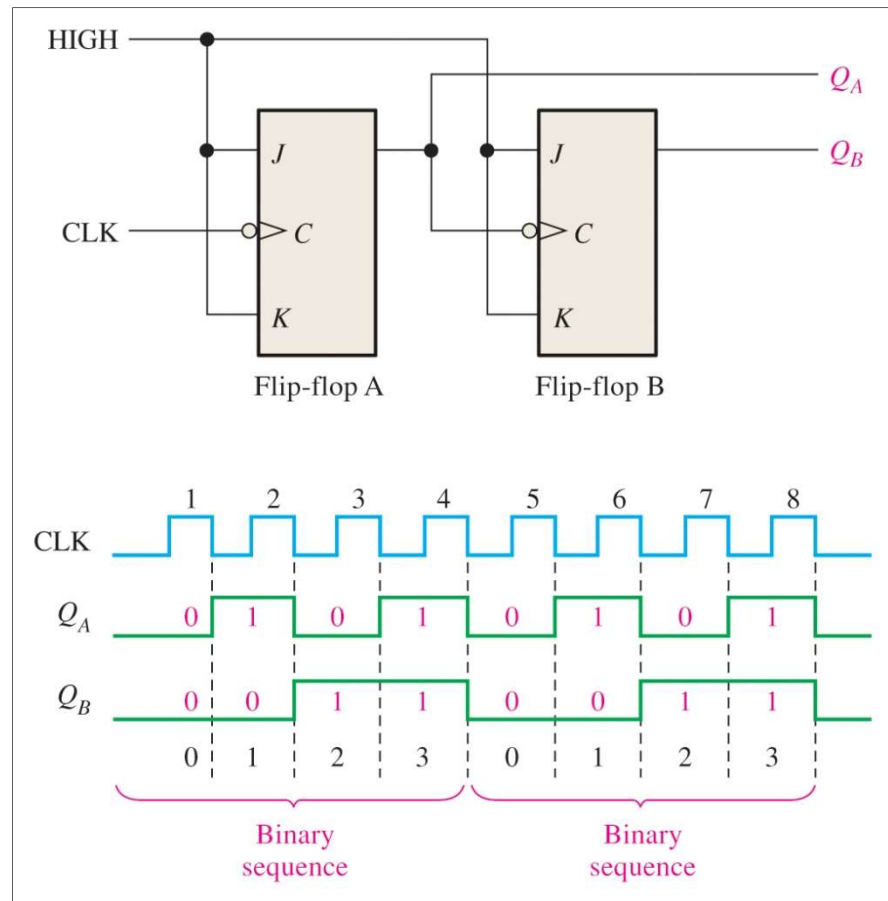
The Q_A and Q_B outputs indicate the number of CLK inputs received.



Ch.7 Summary


One-Shots

 The **one-shot** or **monostable multivibrator** is a device with only one stable state. When triggered, it goes to its unstable state for a predetermined length of time, then returns to its stable state.




Nonretriggerable One-Shots

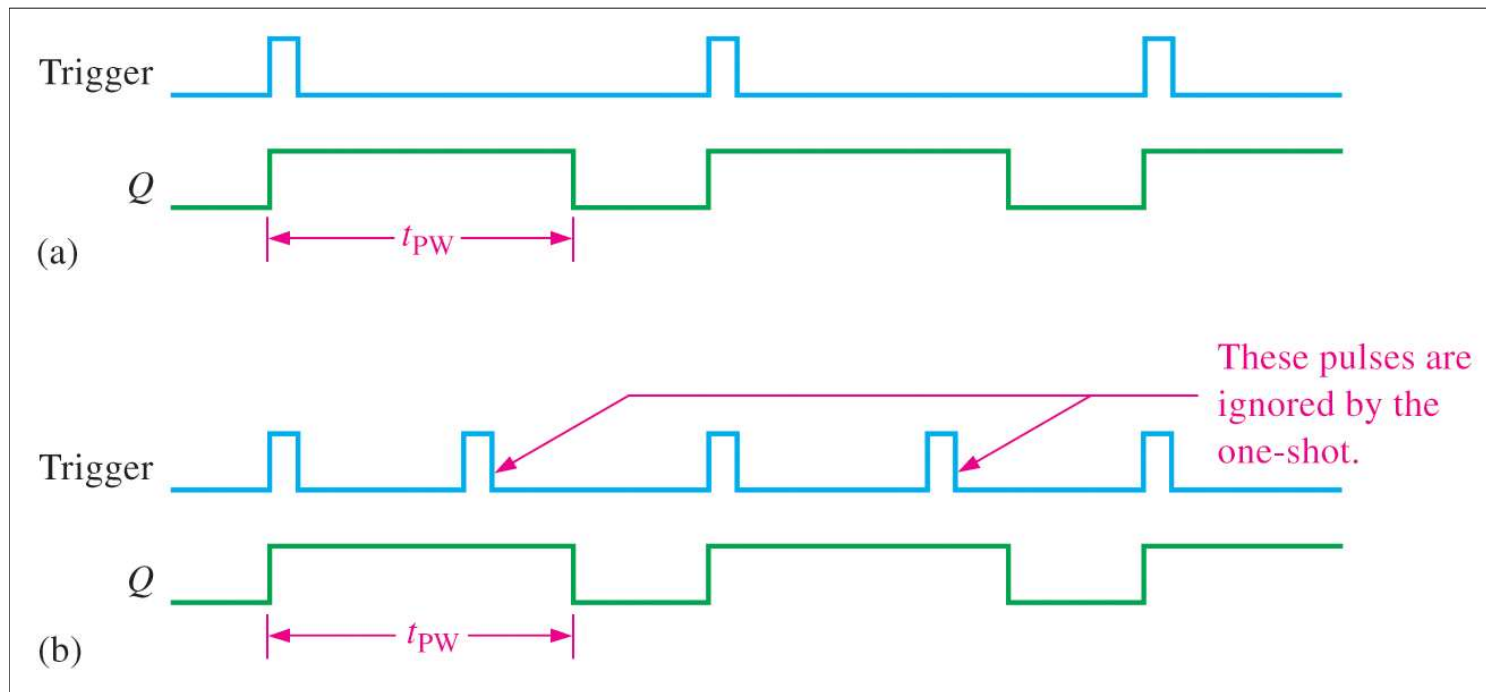A **nonretriggerable** one-shot does not respond to any triggers that occur while in its unstable state, as shown here.



Retriggerable One-Shots

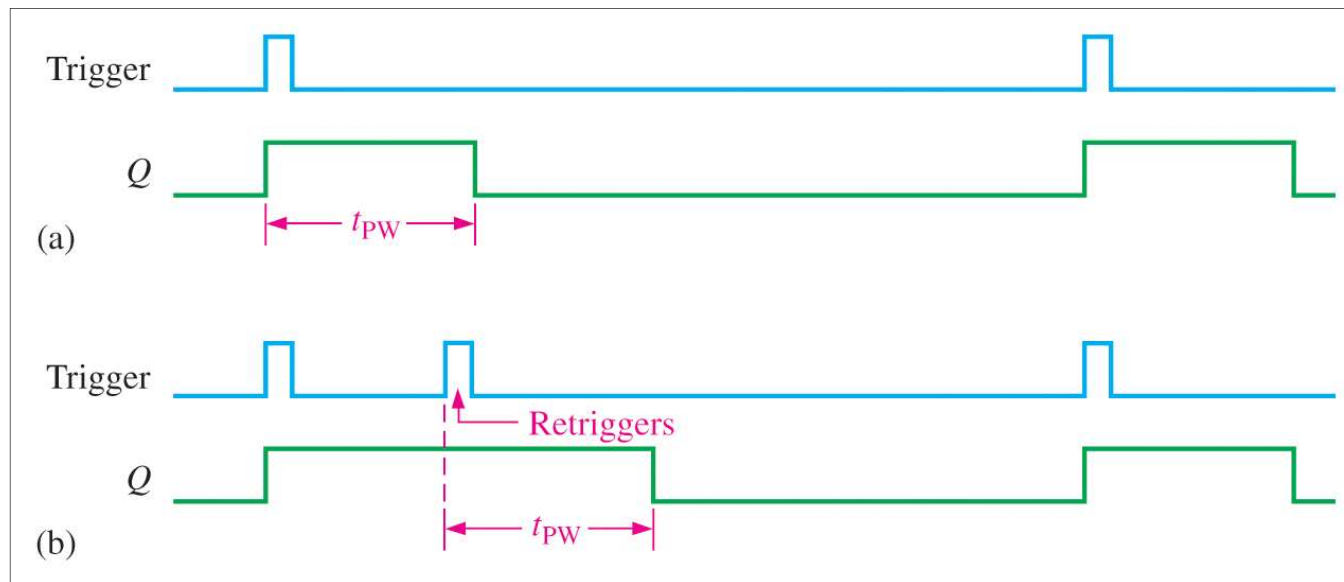Retriggerable one-shots respond to any trigger, even if it occurs while the component is in its unstable state. If it occurs during the unstable state, the state is extended by an amount equal to its normal output pulse width.



Ch.7 Summary

A One-Shot Sequential Timer

One-shots can be wired (as shown) to form a sequential timer; a circuit that can set up a sequence of actions, such as lighting a group of lights in a particular order.

