

Digital Fundamentals


Thomas L. Floyd

Logic Gates /
Boolean Algebra and Logic Simplification
Chapter 3

Ch.3 Summary

The Inverter

Boolean **NOT** operation

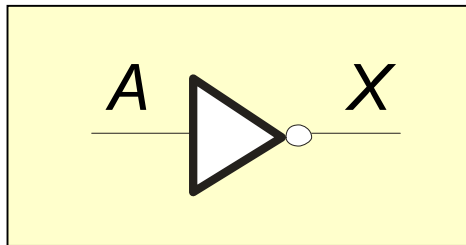


Input	Output
A	X
LOW (0)	HIGH (1)
HIGH (1)	LOW (0)


The **NOT** operation (complement) : $X = \overline{A}$.

Ch.3 Summary


An Inverter Application

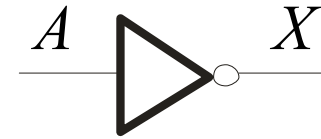

Example waveforms:


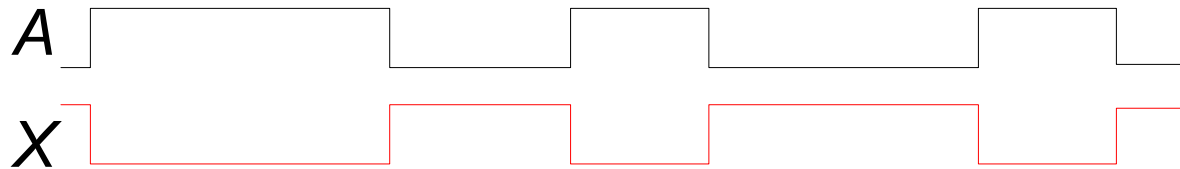


Example: 1's Complement

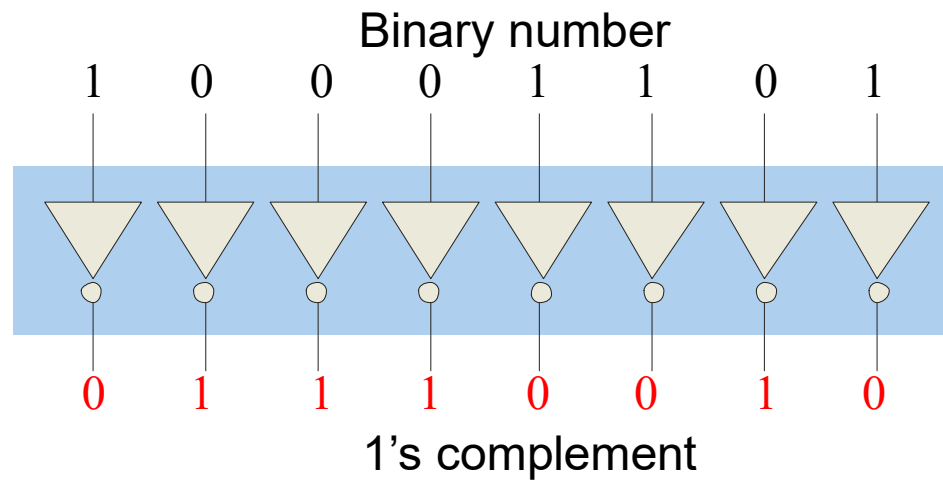

Ch.3 Summary

The AND Gate

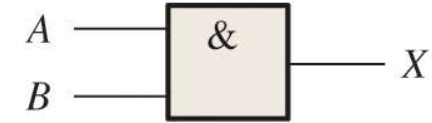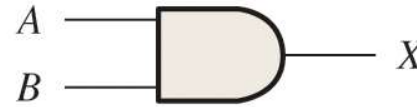



Outputs HIGH when all inputs are HIGH

Inputs		Output
<i>A</i>	<i>B</i>	<i>X</i>
0	0	0
0	1	0
1	0	0
1	1	1


The **AND** operation : $X = A \cdot B$ or $X = AB$.

Ch.3 Summary

The AND Gate

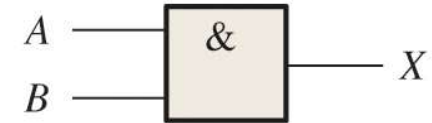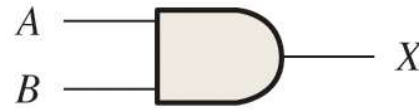

Example waveforms:

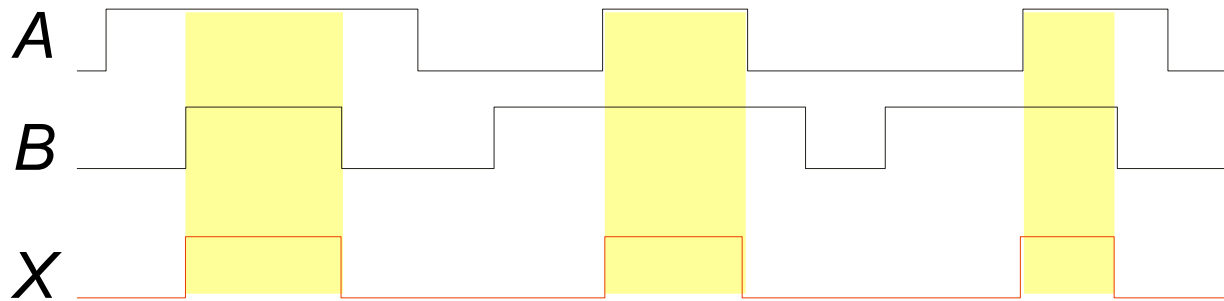



Example: Masking

If the binary number 10100011 is ANDed with the mask 00001111, what is the result?

00000011

Ch.3 Summary

The OR Gate

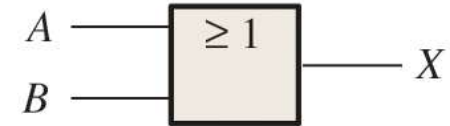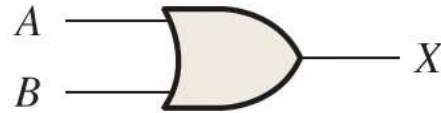



Outputs HIGH if any input is HIGH

Inputs		Output
A	B	X
0	0	0
0	1	1
1	0	1
1	1	1


The **OR** operation : $X = A + B$.

Ch.3 Summary

The OR Gate

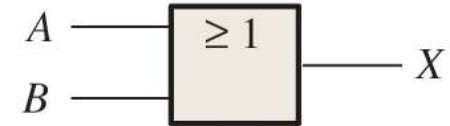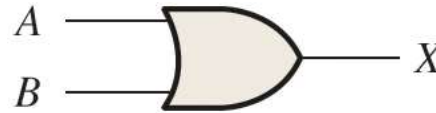

Example waveforms:

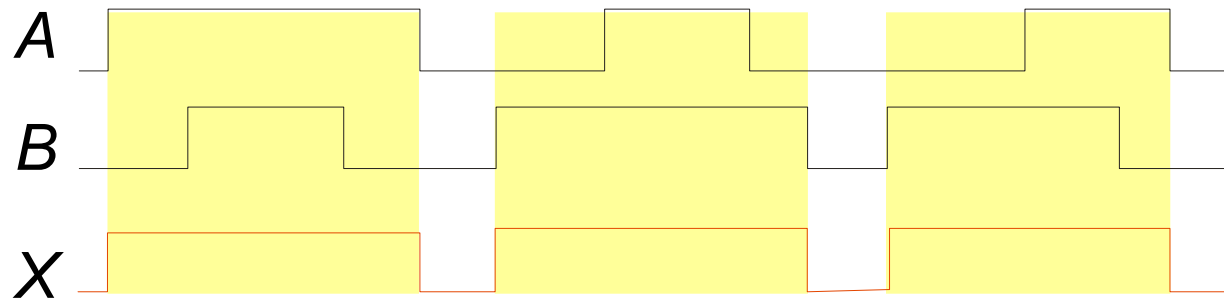

Example: ASCII (Set to specific bit)



5th bit: 1 if lowercase, 0 if uppercase

(ASCII letter) OR (8-bit mask 00100000)?

The resulting letter will be lower case.

Ch.3 Summary

The NAND Gate

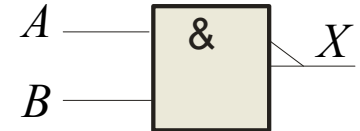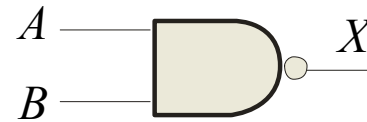



Outputs LOW when all inputs are HIGH

Inputs		Output
A	B	X
0	0	1
0	1	1
1	0	1
1	1	0


The **NAND** operation $X = \overline{A \cdot B}$ (Or, $X = \overline{A} \overline{B}$.)

Ch.3 Summary

The NAND Gate

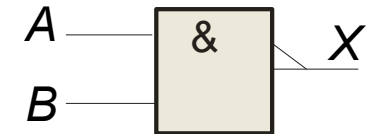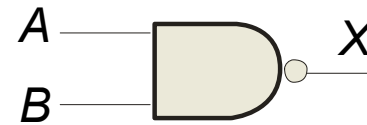


Example waveforms:

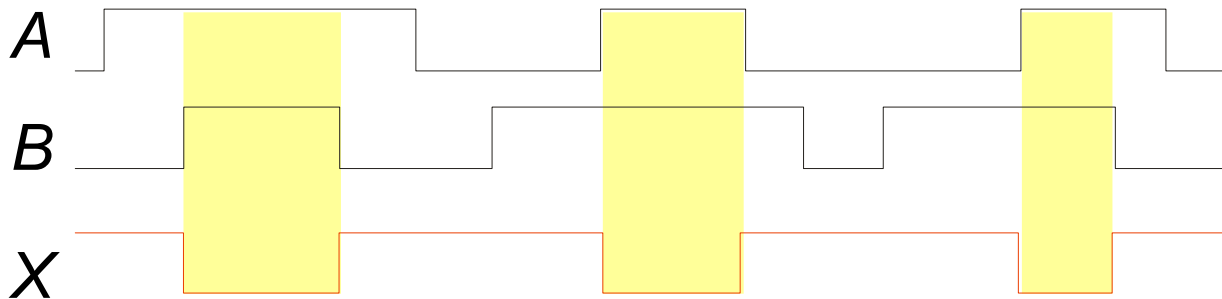

The NAND gate is “universal”.



Inverter using NAND gate:

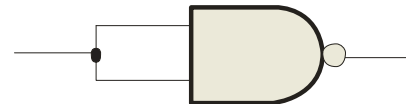

Ch.3 Summary

The NOR Gate

Outputs LOW if any input is HIGH

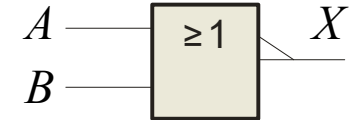
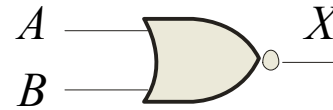


Inputs		Output
<i>A</i>	<i>B</i>	<i>X</i>
0	0	1
0	1	0
1	0	0
1	1	0


The **NOR** operation : $X = \overline{A + B}$.

Ch.3 Summary

The NOR Gate

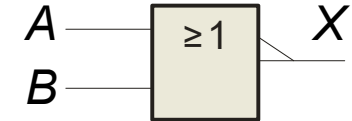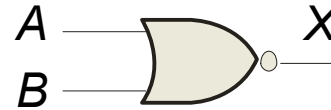


Example waveforms:

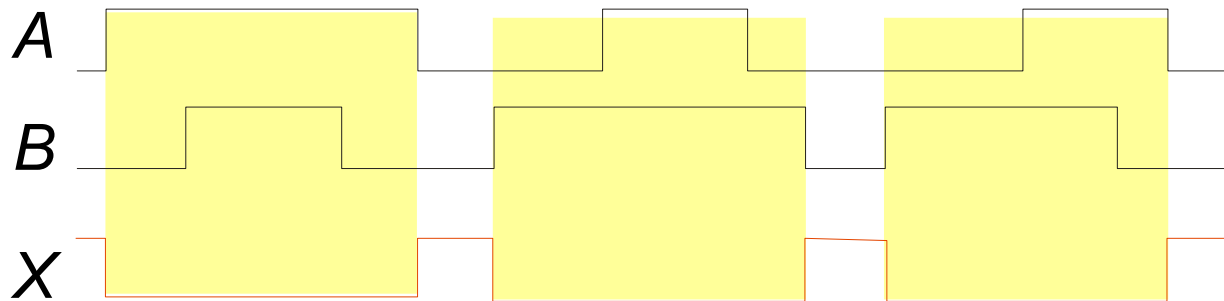

The NOR operation will produce a LOW if any input is HIGH.



When is the LED is ON for the circuit shown?

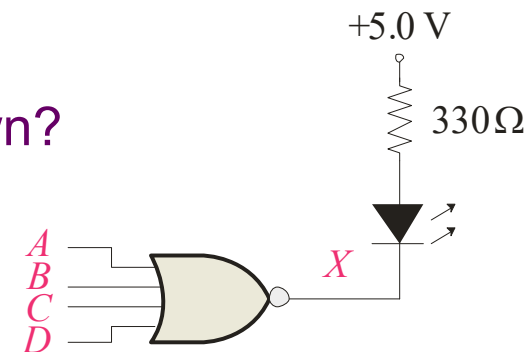The LED will be on when any of the four inputs are HIGH.



Ch.3 Summary

The XOR Gate

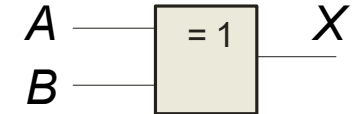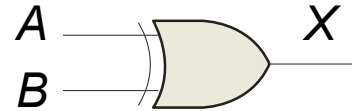



Outputs HIGH only when both inputs are at opposite logic levels.

Inputs		Output
<i>A</i>	<i>B</i>	<i>X</i>
0	0	0
0	1	1
1	0	1
1	1	0


The **XOR** operation : $X = A\bar{B} + \bar{A}B$ or $X = A \oplus B$.

Ch.3 Summary

The XOR Gate

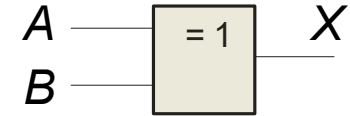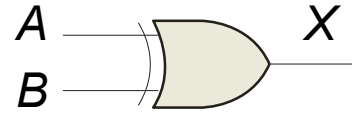

Example waveforms:

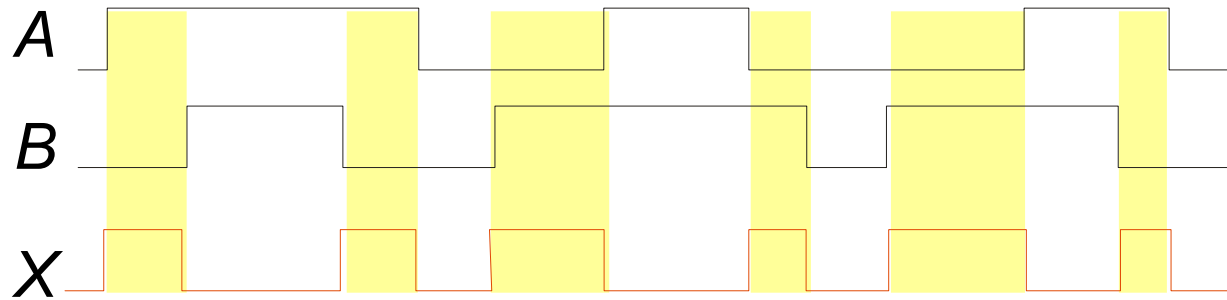



Notice that the XOR gate will produce a HIGH only when exactly one input is HIGH.

If the A and B waveforms are both inverted for the above waveforms, how is the output affected?

There is no change in the output.

Ch.3 Summary

The XNOR Gate

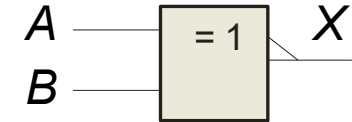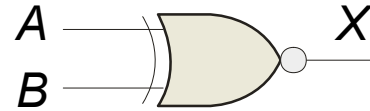



The **XNOR** gate produces a HIGH output only when both inputs are at the same logic level. The truth table is

Inputs		Output
<i>A</i>	<i>B</i>	<i>X</i>
0	0	1
0	1	0
1	0	0
1	1	1


The **XNOR** operation : $X = \overline{A}\overline{B} + AB$ or $X = A \odot B$.

Ch.3 Summary

The XNOR Gate

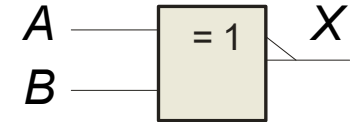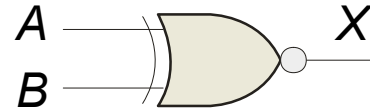

Example waveforms:

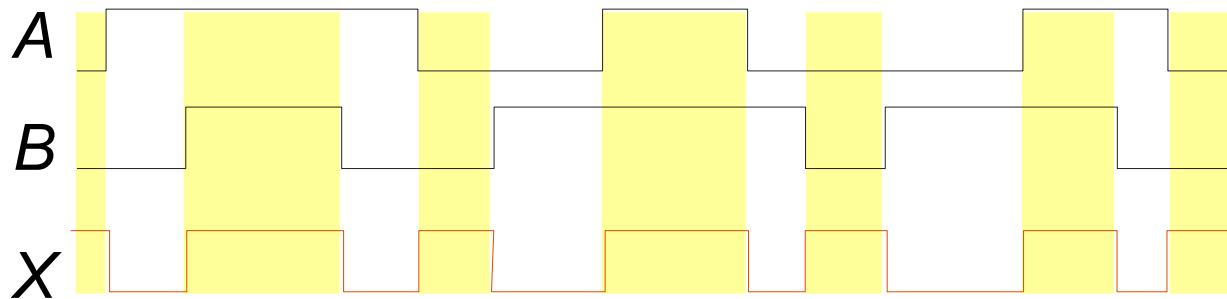

Notice that the XNOR gate will produce a HIGH when both inputs are the same. This makes it useful for comparison functions.

If the A waveform is inverted but B remains the same, how is the output affected?

The output will be inverted.

Ch.3 Summary

Fixed Function Logic

