

**Digital Circuits**  
**Final, Friday May 28th**

**Instructions:**

- You have **three hours**, 7PM - 10PM
- The exam has 6 questions, totaling 170 points.
- You are allowed to carry the textbook, your own notes and other course related material with you. Electronic reading devices are not allowed.
- You are required to provide a detailed explanation of how you arrived at your answers.

**Class :** \_\_\_\_\_

**ID :** \_\_\_\_\_

**Name :** \_\_\_\_\_

1	/ 20
2	/ 40
3	/ 20
4	/ 30
5	/ 30
6	/ 30
<hr/>	
Total	/ 170

# 1. Waveforms (20 points)

Determine the waveform of the output. No need to justify the answer.

- (a) Consider the 2-bit decoder where all inputs and outputs are ACTIVE-HIGH. (10 points)

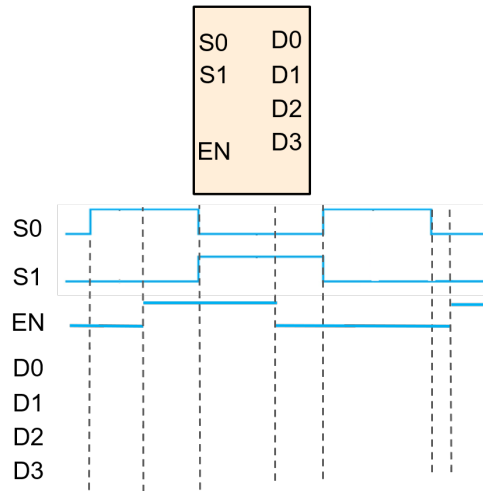


Figure 1: Problem 1(a).

- (b) Assume initially  $Q_0 = Q_1 = Q_2 = Q_3 = 0$  where all flip flops are positive edge triggered. (10 points)

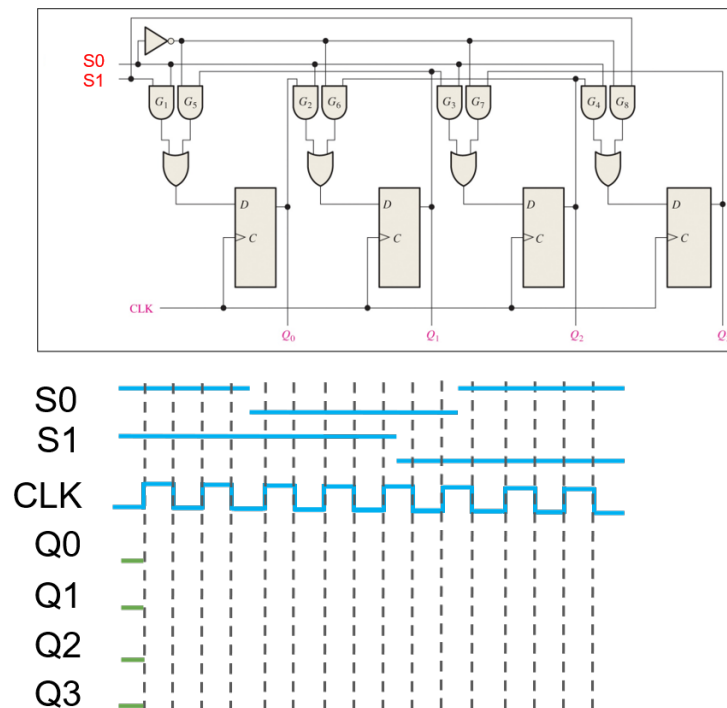


Figure 2: Problem 1(b).

## 2. Mix of Problems (40 points)

Answer the following questions. You have to justify your answer.

(a) Show that XOR operation is associative. (10 points)

(b) Show that NOR operation is not associative (10 points)

(Hint: It is enough to show that  $(A \text{ NOR } B) \text{ NOR } C \neq A \text{ NOR } (B \text{ NOR } C)$  for some  $A, B, C$ )

- (c) Construct  $X = ABD + \bar{A}C$  with 5 NOR gates only. You are NOT allowed to use any other gates (Inverter is NOT allowed as well). *(10 points)*  
(Note: your NOR gates can take as many input as you want)

- (d) Consider a 4-bit comparator that compares  $A = A_3A_2A_1A_0$  and  $B = B_3B_2B_1B_0$  is given. It outputs  $G$  ( $G = 1$  iff  $A > B$ ),  $E$  ( $E = 1$  iff  $A = B$ ), and  $L$  ( $L = 1$  iff  $A < B$ ). Use this 4-bit comparator, design a digital block for  $X$  that checks whether  $C \geq 2 \times D$  where  $C = C_3C_2C_1C_0$  and  $D_3D_2D_1D_0$ . In other words,  $X = 1$  if and only if  $C \geq 2 \times D$ . You are allowed to use additional input (VCC, GND) and gates, but your final design should be minimized.

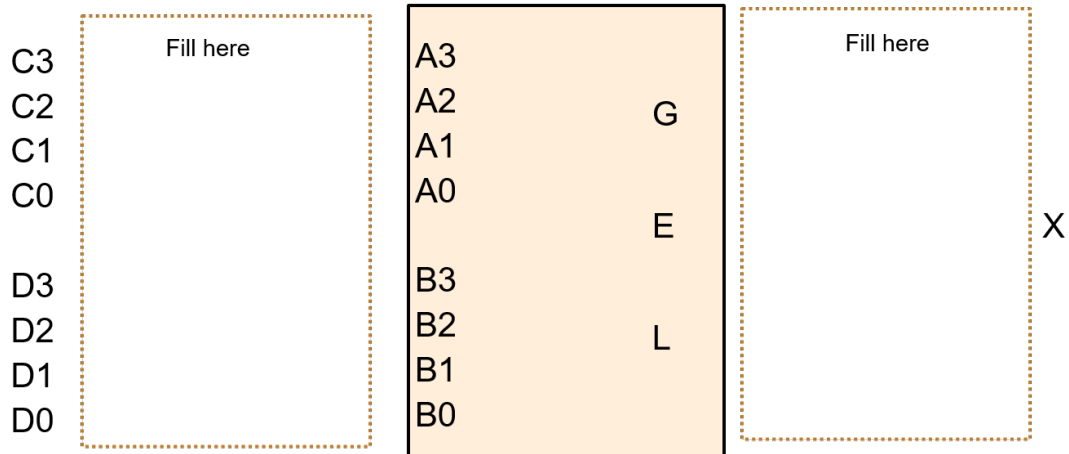


Figure 3: Problem 2(d).

**3. Count the Number of Leading Zeros** (20 points)

Design a digital block which counts the number of leading zeros of 4-bit binary number. In this design, assume that only AND, OR, NOT gates are available. More precisely, the input signal  $A$  has four bits  $A_3A_2A_1A_0$  and the output signal  $B$  has five bits  $B_4B_3B_2B_1B_0$ . If the number of leading zero is  $k$ , then  $B_k = 1$  and all other  $B$ 's are zero. For example, if  $A_3A_2A_1A_0 = 0110$ , then  $B_4B_3B_2B_1B_0 = 00010$ , and if  $A_3A_2A_1A_0 = 0001$ , then  $B_4B_3B_2B_1B_0 = 01000$ . We call this block by "4-bit leading zero counter".

- (a) Reduce  $B_0, B_1, B_2, B_3, B_4$  to minimum SOP forms. (10 points)  
(Hint: if you can get correct forms with reasonable explanation, you do not have to draw a Karnaugh map.)
- (b) Using the above block, design another digital block which counts the number of leading zeros of 8-bit binary numbers, where the input signal has eight bits  $A_7A_6 \cdots A_0$ , and the output signal  $B$  has nine bits  $B_8B_7 \cdots B_0$ . You are allowed to use two "4-bit leading zero counter" blocks, and additional AND, OR, NOT gates. (10 points)

Problem 3 continued.

**4. Flip Sign** (30 points)

Design a 4-bit sign converter which takes  $A = A_3A_2A_1A_0$  as an input, and the output  $B = B_3B_2B_1B_0$  is a two's complement of  $A$ . For example, if  $A_3A_2A_1A_0 = 1010$ , then  $B_3B_2B_1B_0 = 0110$ .

- (a) Draw truth tables for each output  $B_3, B_2, B_1, B_0$ . (10 points)  
(Hint: you can always apply “two's complement operation” even in the case where we cannot convert the sign in two's complement number system.)
- (b) Reduce each output  $B_0, B_1, B_2, B_3$  to minimum SOP form. You may want to use Karnaugh map. (10 points)
- (c) In two's complement number system, there exists a number which we cannot convert the sign. Let  $E$  be the output to indicate whether we cannot convert the sign of input, i.e.,  $E = 1$  if we cannot convert the sign of  $A = A_3A_2A_1A_0$ . Describe the Boolean expression for  $E$  using input signal  $A_3, A_2, A_1, A_0$ . (10 points)



Problem 4 continued (1/2).

Problem 4 continued (2/2).

### 5. Mealy Machine (30 points)

Design a 3-bit up/down counter using JK flip-flops with input  $X$  where the state is under 2's complement system. If  $X = 0$ , it counts  $-4, -3, -2, -1, 0, 1, 2, 3, -4, -3, \dots$ . If  $X = 1$ , it flips the sign  $3 \leftrightarrow -3$ ,  $2 \leftrightarrow -2$ , and  $1 \leftrightarrow -1$ . If  $X = 1$  and the current state is 0 or -4, the state remains the same, i.e.,  $0 \rightarrow 0$ , and  $-4 \rightarrow -4$ . For example,

- If the current state is 001 and  $X = 0$ , then the next state is  $B = 010$ .
- If the current state is 101 and  $X = 1$ , then the next state is  $B = 011$ .
- If the current state is 000 and  $X = 1$ , then the next state is  $B = 000$ .

(a) Draw a state diagram. (5 points)

(b) Fill the next-state table. (5 points)

(c) Draw the JK flip-flop transition table. (5 points)

(d) Draw the Karnaugh maps. (5 points)

(e) Show the logic expressions in minimum SOP forms. (5 points)

(f) Implement the counter. (5 points)

You are allowed to use JK flip flops, AND, OR, NOT, XOR, XNOR gates. You do not need to specify PRE or CLR of flip flops.

Problem 5 continued (1/2).

Problem 5 continued (2/2).

## 6. Elevator (30 points)

Design a simple elevator controller using D flip-flops. Suppose the elevator can be in one of four states, depending on whether it is on the 1st or 2nd floor, and whether its door is closed or open. It can take in two inputs, one for the close/open door button, and the other for the up/down button.

- Let  $S_1$  represent the floor that the elevator is on, either 1st ( $S_1 = 0$ ) or 2nd ( $S_1 = 1$ ). Let  $S_0$  represent whether the door is closed ( $S_0 = 0$ ) or open ( $S_0 = 1$ ).
  - For example,  $S_1S_0 = 01$  is the state in which the elevator is open on the 1st floor.
- Let  $I_1$  represent the button to go either down (0) or up (1). Let  $I_0$  represent the close (0) or open (1) door button.  $I_1$  takes action before  $I_0$ .
  - For example,  $I_1I_0 = 11$  tells the elevator to go up a floor and open the door.
- If we try to go up from the 2nd floor or go down from the 1st floor, the elevator does not move.
- The elevator can only move if its door is closed ( $S_0 = 0$ ). If we try to move the elevator while the door is open, it stays in the same floor (but the  $I_0$  will be applied).
  - For example, if the elevator is on the 1st floor and door is opened, with  $I_1 = 1$  (up) and  $I_0 = 0$  (close), the elevator will stay on the 1st floor but the door will be closed.

- (a) Draw the state diagram with all four states  $S_1S_0$  and all possible inputs  $I_1I_0$  for each state. (5 points)
- (b) Fill the next-state table. (5 points)
- (c) Draw the D flip-flop transition table. (5 points)
- (d) Draw the Karnaugh maps of  $D_0$  and  $D_1$ . (5 points)
- (e) Show the logic expressions for  $D_0$  and  $D_1$  in minimum SOP forms. (5 points)
- (f) Implement the elevator using two D flip-flops and logic gates. (5 points)  
You do not need to specify SET or RESET of flip flops.

Problem 6 continued (1/2).

Problem 6 continued (2/2).